
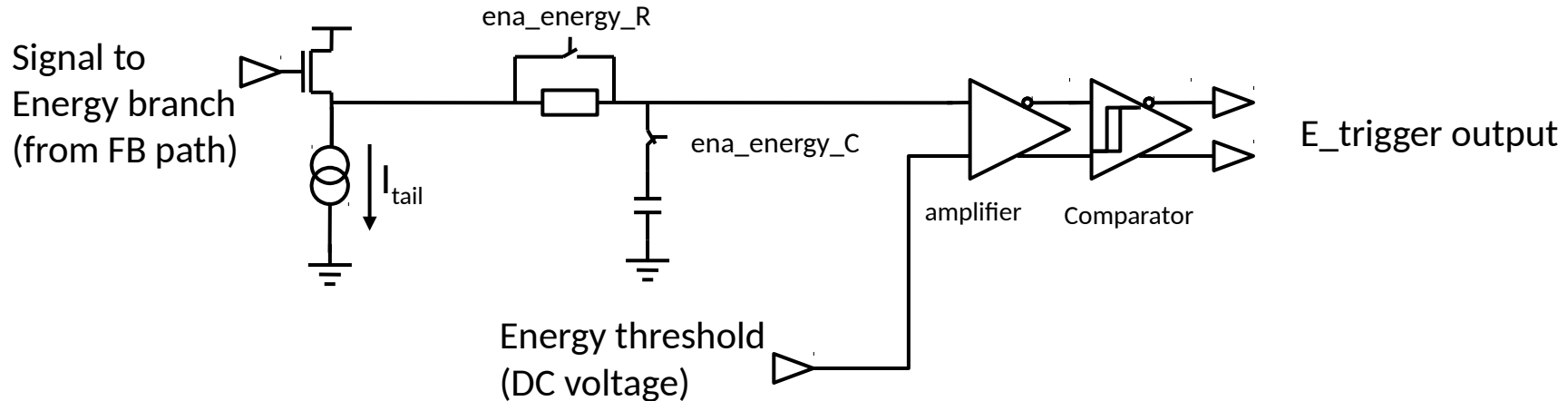
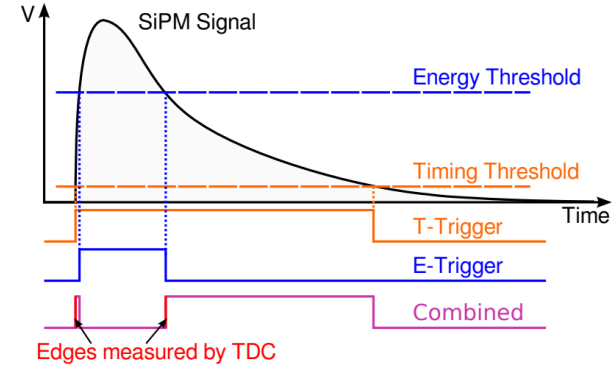


# MuTRiG Energy Branch Modification (for Mu3e Fibre Detector)
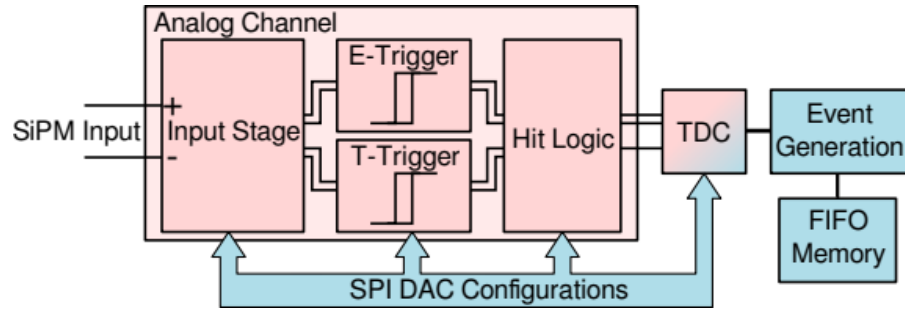
# Introduction of MuTRiG analog part and energy branch




# Problems and requirements

- With RC-filter, few-photon event signals have **too small amplitude** to trigger the energy branch.
- Without RC-filter, the energy trigger signals are **too short** such that the second edge of the combined signal falls into the dead time of TDC and is not registered by TDC.

## Requirements:


1. To distinguish DCR event and physical event
  2. To integrate the signals for the photons from the same event which might come with certain arrival time difference (5ns)
- The energy branch should be triggered by 1-photon event.
  - The energy trigger signals should be longer than TDC dead time.
  - The energy branch should have sufficient resolution to distinguish 1-photon event and 2-photon event.

# Single-photon signal with RC filter On

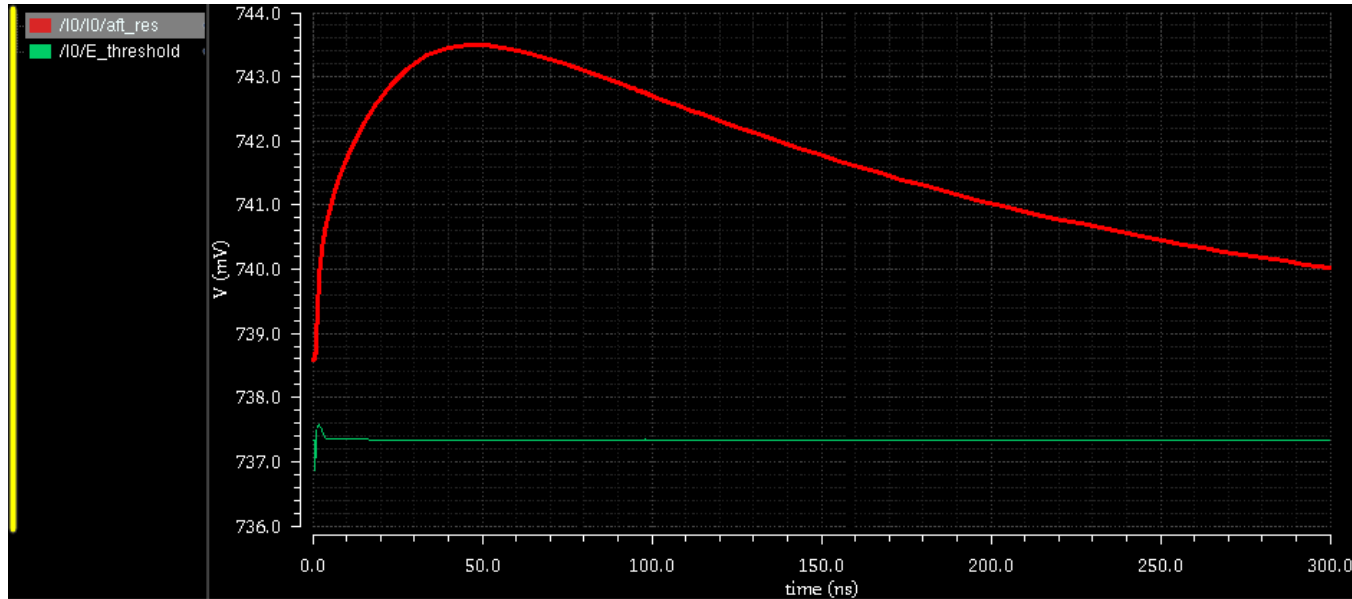

- Amplitude:  $\sim 5\text{mV}$ .
- Less than LSB of energy threshold DAC ( $\sim 7\text{mV}$ ).


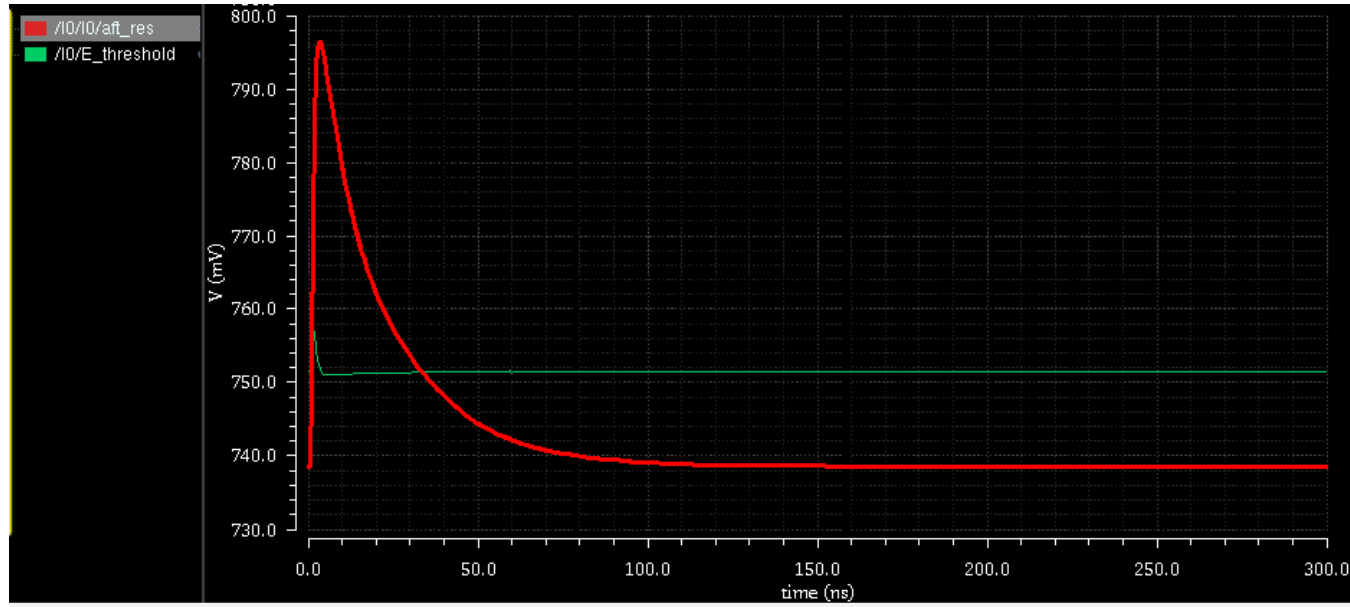
# Single-photon signal with RC filter off



- Amplitude:  $\sim 60\text{mV}$ .
- Pulse is too short.

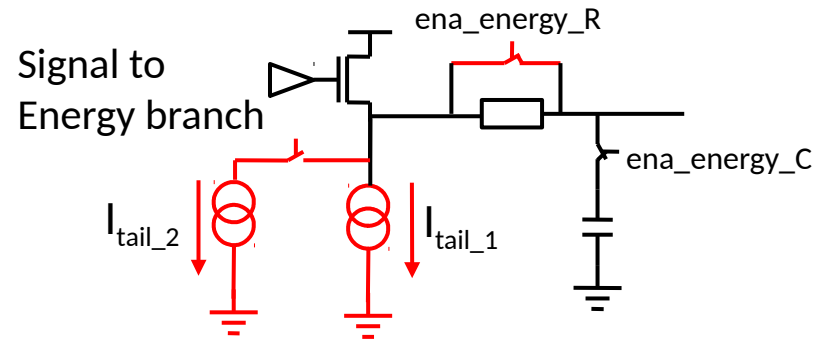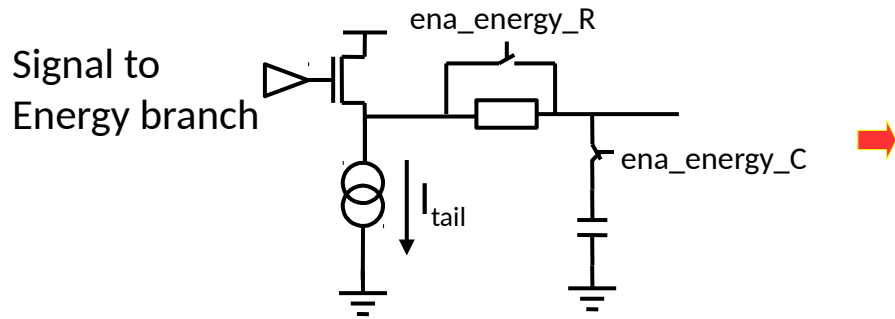
# Solution

- Short the Resistor
  - Reduce the bias current of previous source follower stage
  - Add a switch to restore the original configuration
- extend the tail of the signal




- Small  $I_{tail_1}$
- $I_{tail_1} + I_{tail_2} = I_{tail}$


# Signals for 1-5 photons events

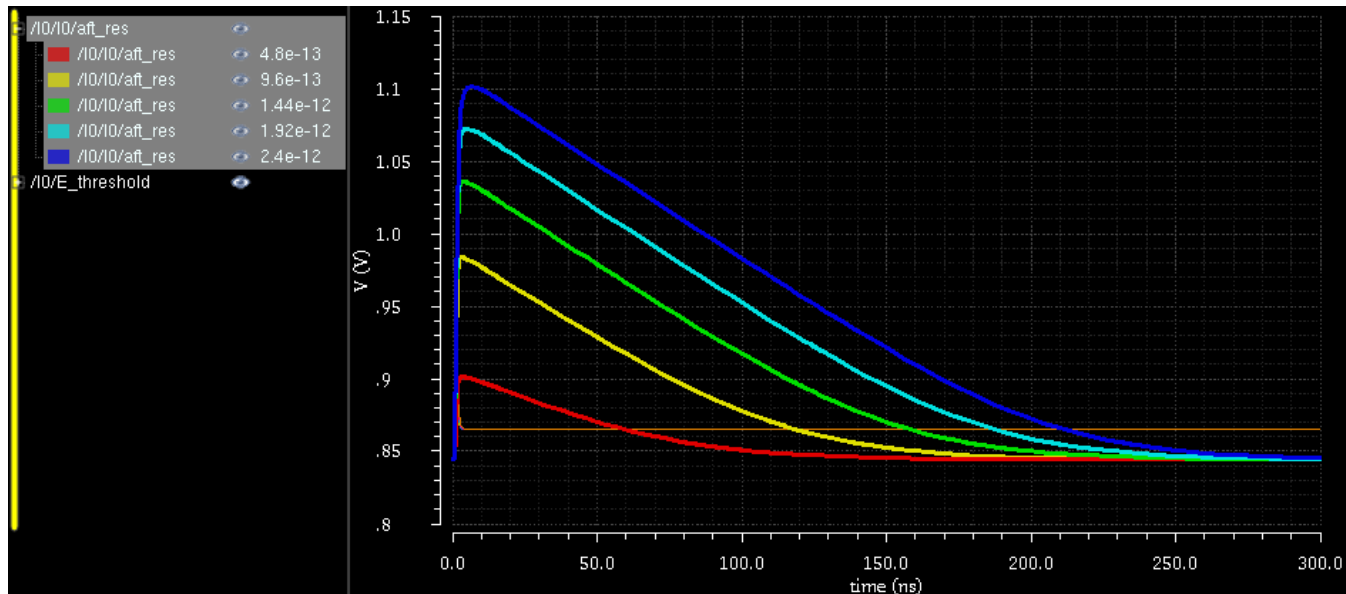

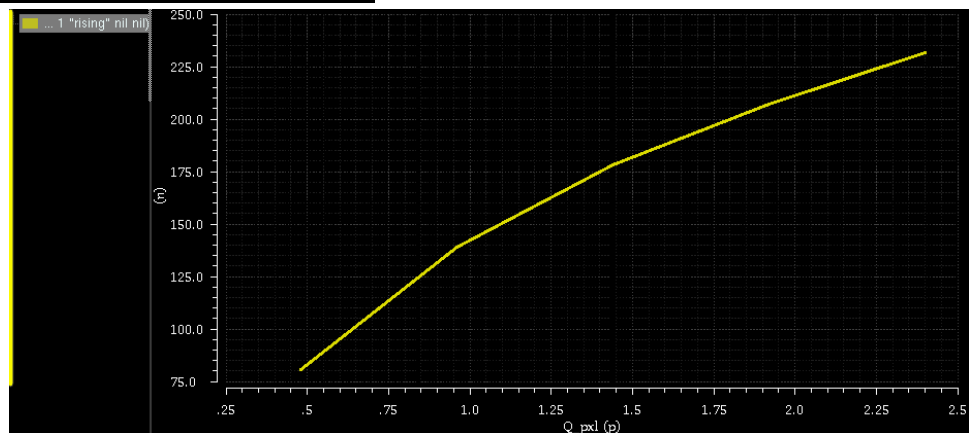- Amplitude: 50 – 250mV ( covered by 7-30 E threshold DAC values)
- ToT pulse width: 80 – 230 ns



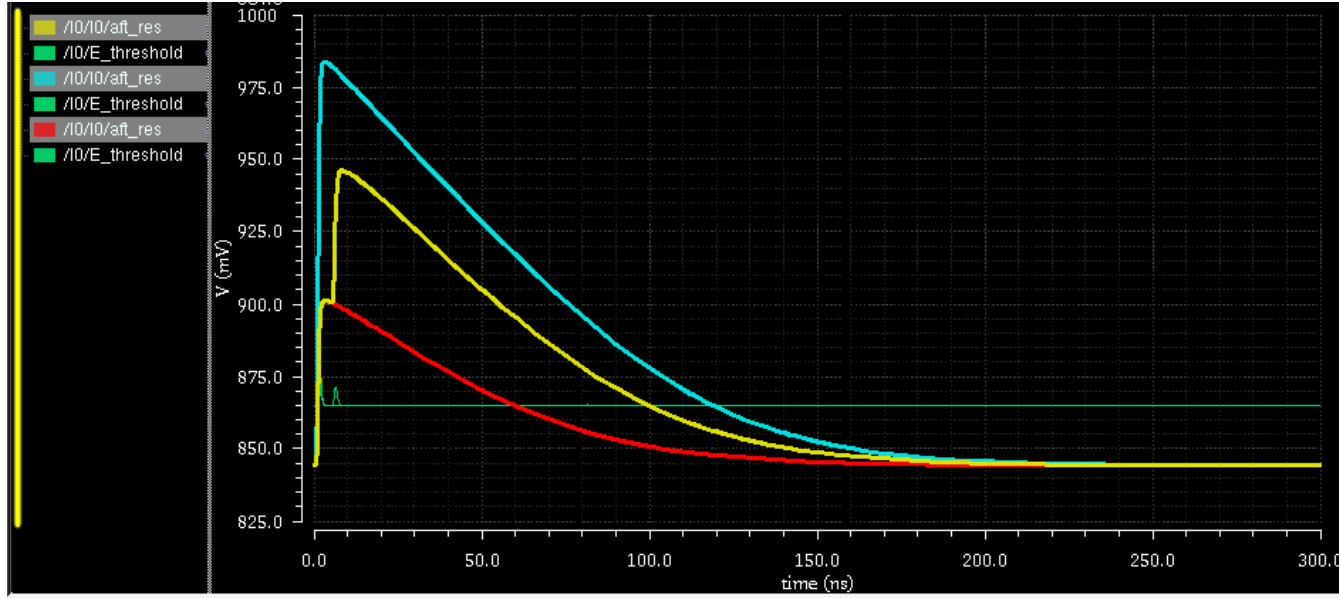
# Signal with 2 photons separated by 5 ns



Case	ToT (ns)
1-photon	80
2-photon (5n separation)	120
2-photon (at the same time)	139



# Layout Plan

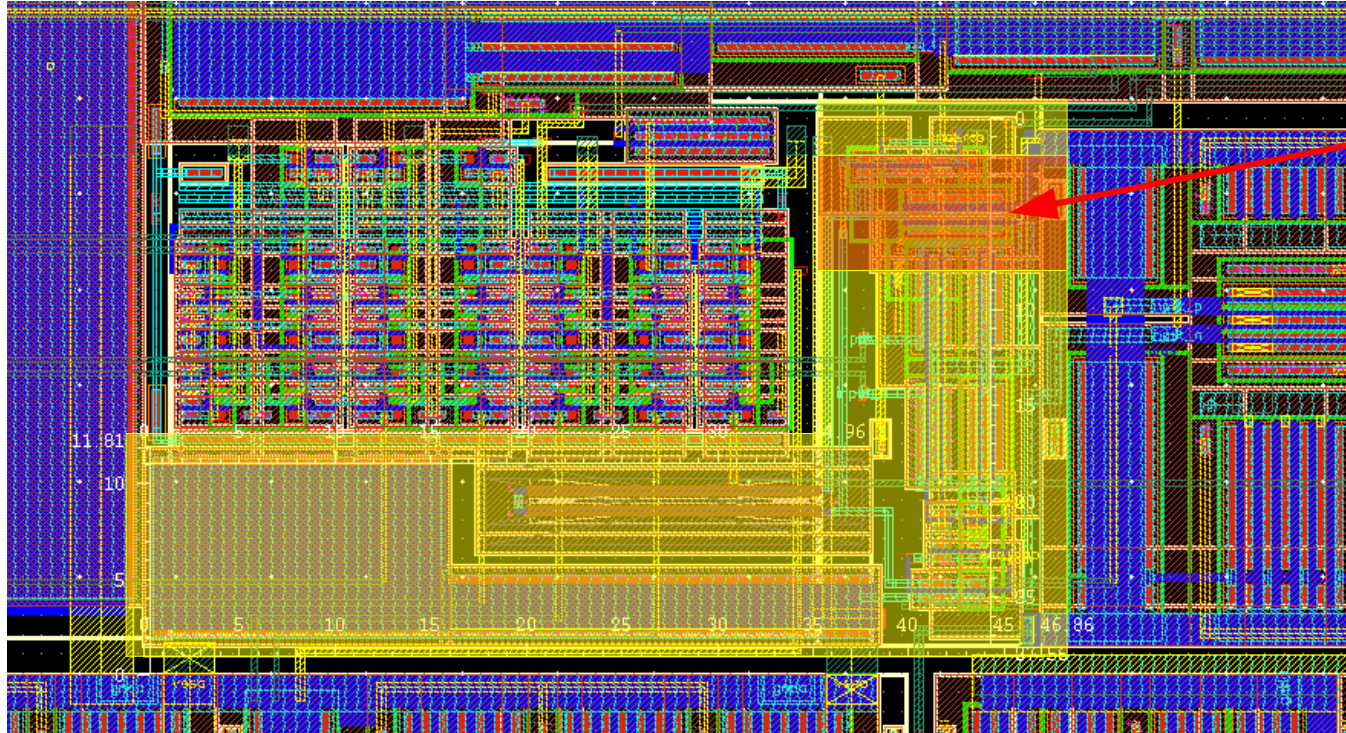

- Add a switch here (one more SPI bit).
- Add a small transistor here.

# Further Modifications

- De-couple the energy threshold and timing threshold?