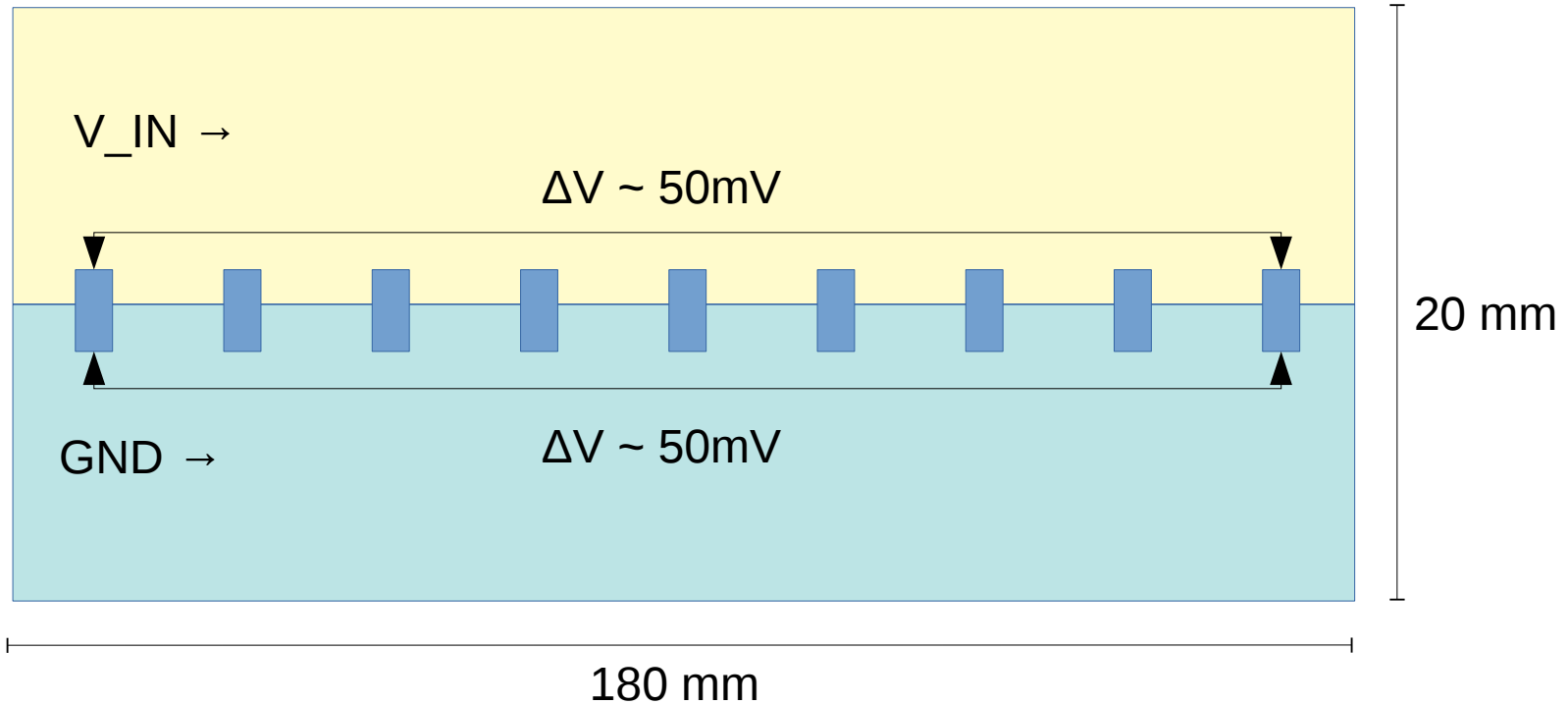



“Naive” Routing



- The “naive” routing scheme **minimizes** overall the power loss: $P_{\text{loss}} = 375\text{mW}$
- The summed voltage drop between sensor 1 and 9 is $2 \times 50 = 100\text{mV}$

$$P_{\text{loss}} = 2 \cdot R_0 (I_0)^2 \cdot g, \quad R_0 = 2.2\text{m}\Omega, \quad I_0 = 0.5\text{A}, \quad g = 342 \text{ (geometrical factor)}$$


“Equal Resistance” Routing

 

- The “naive” routing scheme avoids voltage drops between chips;
 $\Delta V = 0\text{mV}$, $V_{\text{loss}} = 2 \times 50\text{mV}$
- Power loss is about **450mW**

$$P_{\text{loss}} = 2 \cdot R_0 (I_0)^2 \cdot g, \quad R_0 = 2.2\text{m}\Omega, \quad I_0 = 0.5\text{A}, \quad g = n \cdot n(n+1)/2 = 405 \text{ with } n=9$$


“Telemann” Routing

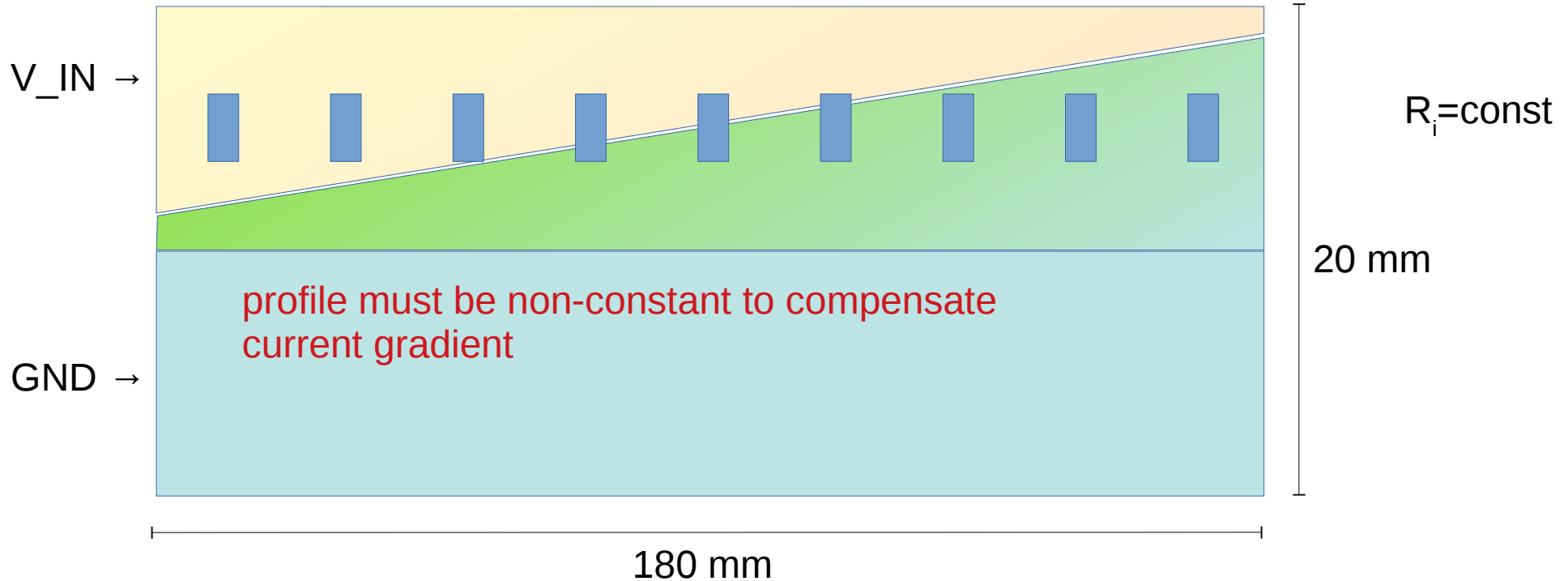

- This routing scheme **avoids** relative voltage drops between chips; but relative large voltage loss of $V_{\text{loss}} = 2 \times 90\text{mV}$, all chips on slightly different potential
- Power loss is about **800 mW**


$$P_{\text{loss}} = 2 \cdot R_0 (I_0)^2 \cdot g, \quad R_0 = 2.2\text{m}\Omega, \quad I_0 = 0.5\text{A}, \quad g = n \cdot n^2 = 729 \quad \text{with } n = 9$$

“Hybrid” Routing

 


Mixture of “naive”, “equal” and “teleman” methods

Applied on HDI Design

 

possible and easy!

Richard's Slide

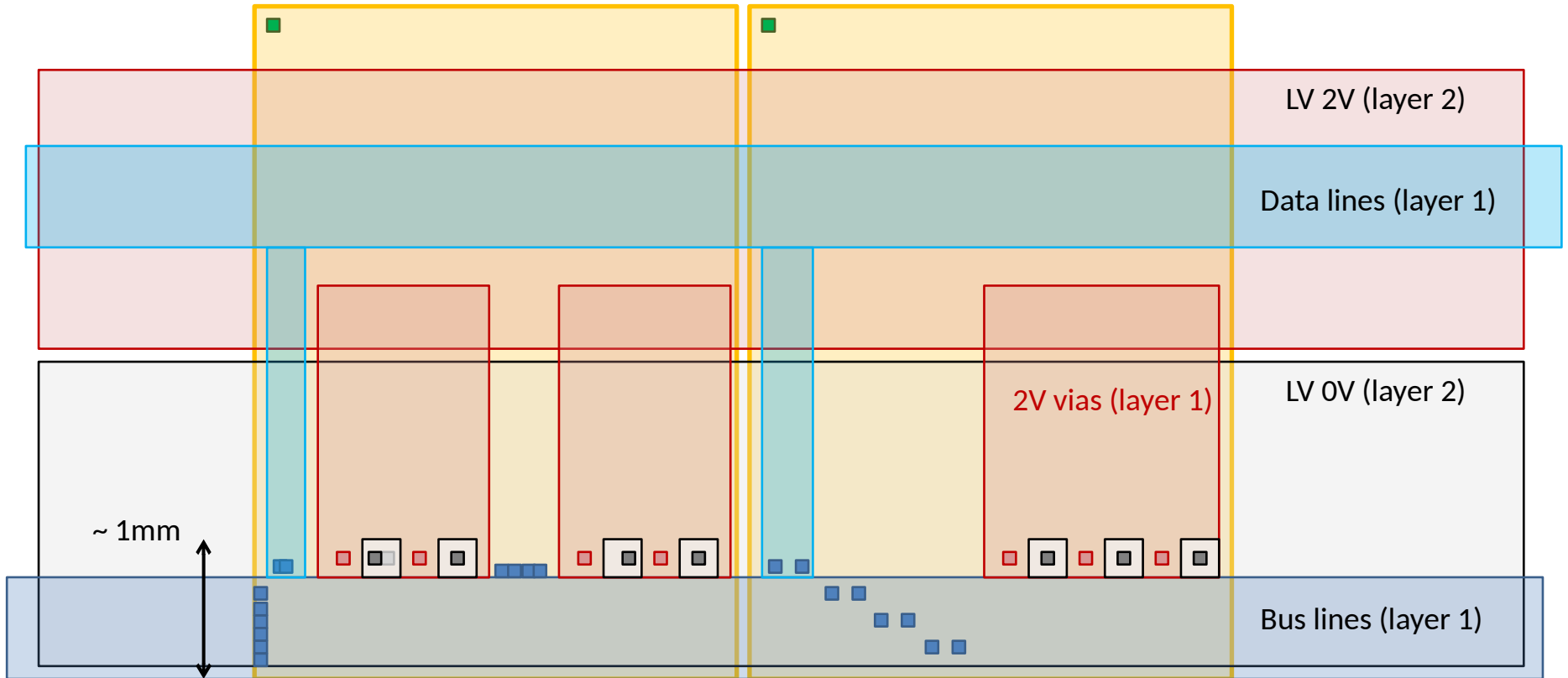

Summary

- Voltage drops can be avoided by simple HDI design changes
- Exact area proportions to be simulated

Backup

Summary Table

Routing schemes:

- 1) Naive Routing → needs 2 SF (no Zener) for all currents to level out voltage drops
- 2) Equal Resistance → needs 1 SF for all PLL and VSSA
- 3) Teleman → dito
- 4) Hybrid (Combination of 2.+3.) → dito




Scheme	P_{loss} (HDI)	#SF current	P_{loss} (SF) per chip	P_{loff} (total)	normalised to 9 Watt
Naive	375 mW	2 x 430mA @0.2-0.5V 2 x 70mA @0.8V	170-430 mW 110 mW	2.9-5.2 W	32% - 58%
Equal	440 mW	1 x 70mA @0.8V	56 mW	0.95 W	11%
Teleman	800 mW	1 x 70mA @0.8V	56 mW	1.30 W	14%

Pixel Tracker Voltage Drops and Power Consumption

- Voltage drops on LTU-HDI due to ohmic resistance
 - spec. resistance $\rho_{\text{alu}} = 2.65 \cdot 10^{-2} \Omega \text{ mm}^2/\text{m}$ (2.8?)
 - trace width 10mm, thickness 12 μm → **2.2m Ω /cm** (oxide?)
 - Mupix power MPV=250 mW/cm² for V=2V, area=4cm² → $I_{\text{Mupix}}=0.5\text{A}$ (rough estimated)
- Voltage loss in 10mm wide trace over full ladder (18cm) for 9 Mupix is **$U_{\Delta} = 200\text{mV}$** (defines scale and worst case scenario)
- Counter measures:
 - improve HDI routing
 - use on chip voltage regulators to compensate voltage drops
- Goal: Minimize voltage drops (→ reliability) and total power consumption (→ cooling)
- Note: power consumption is the results of **loss** in traces and **voltage regulators!**

On chip Voltage Regulators

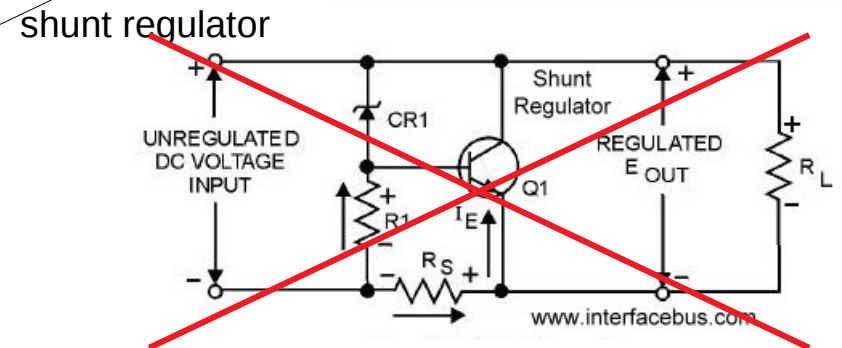  - Purpose of voltage regulators:
 - ➔ regulate voltage (mitigate power drops)
 - ➔ stabilize voltage
- Types of voltage regulators:
 - Zener diode
 - source follower
 - shunt (for serial powering only)
- For parallel powering (Mu3e) the source follower design is best suited
- However voltage drop of **0.2-0.5V** per SF!



Mupix Voltage Stabilization

Remark: I define a voltage as “stable” if it is stable against GND (noise is filtered out).
If GND is noise the voltages must see the same noise!

digital VDD=1.8V:	→ level critical	~190 mA
analog VDDA=1.8V:	→ level critical	~140 mA
amplifier VSSA=1.0V:	→ stable!	~65 mA
LVDS driver:		~15 mA /per link
PLL:	→ stable!	small

- Life becomes easier if on PLL and VSSA are stabilized using voltage regulators
- Could work if voltage levels are stabilized by clever HDI routing