




UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386




Power Regulator on ATLASPix3

Alena Weber

 
ASIC and Detector Laboratory, Karlsruhe Institute of Technology and University Heidelberg




Schematics of the power regulator

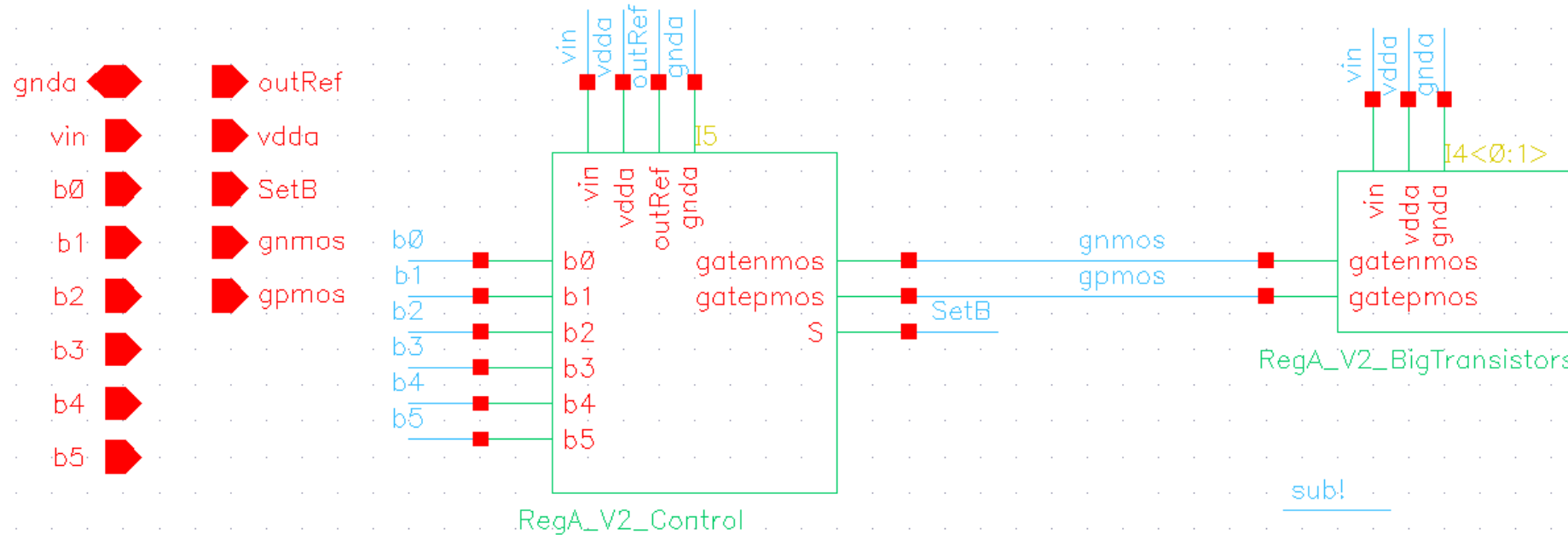


Schematics of the power regulator

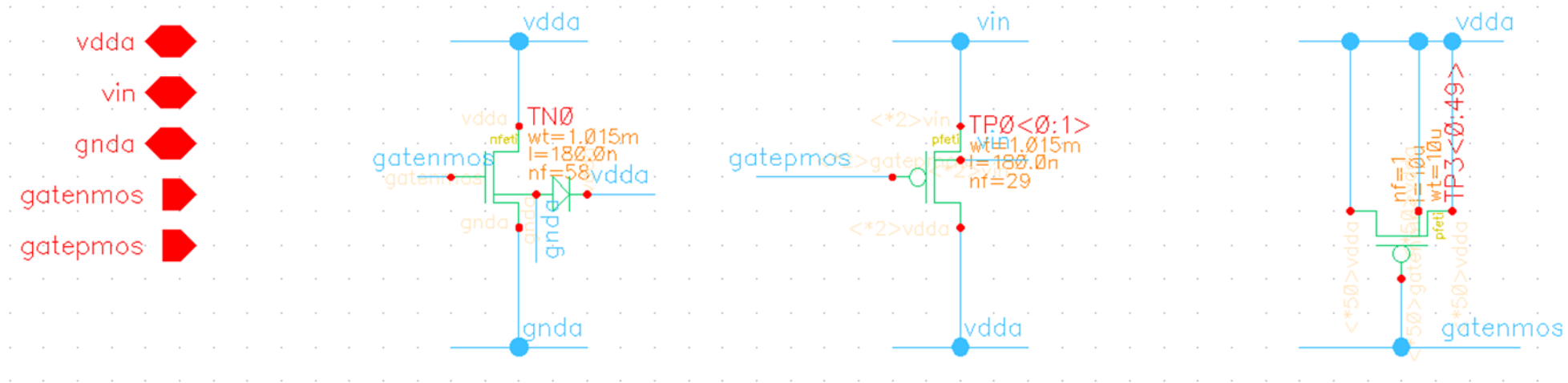


Schematics of the power regulator

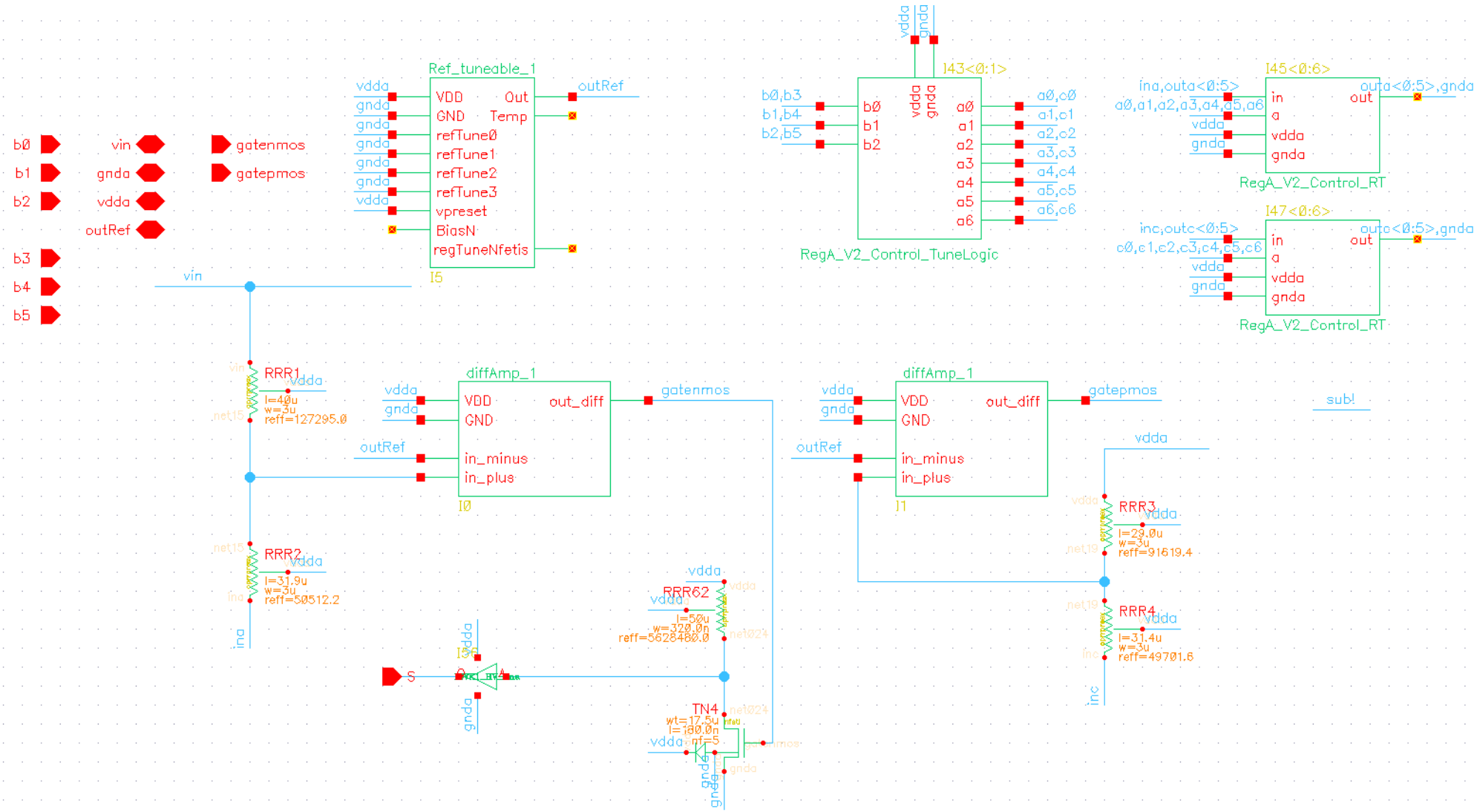

Schematics of the power regulator

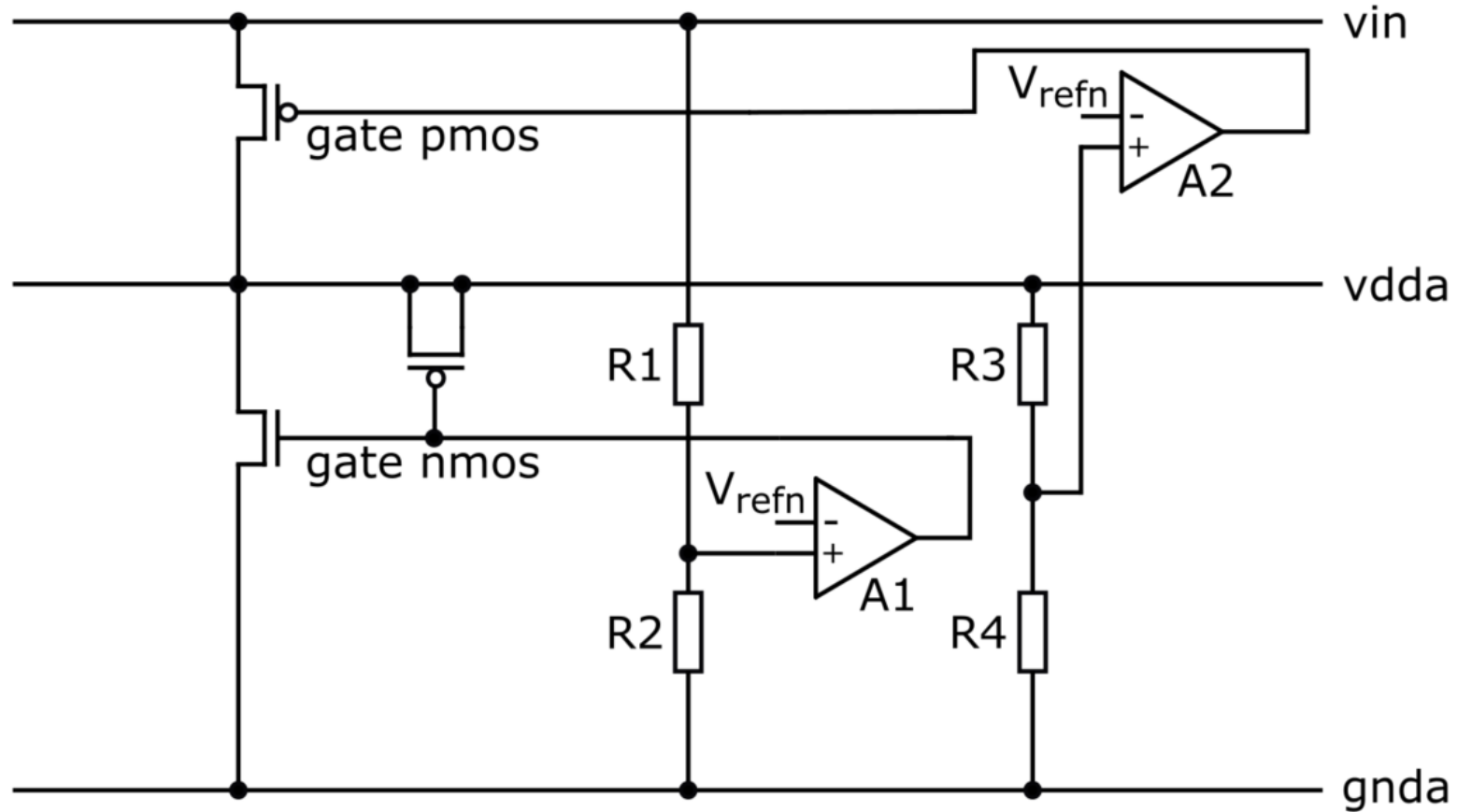

Schematics of the power regulator

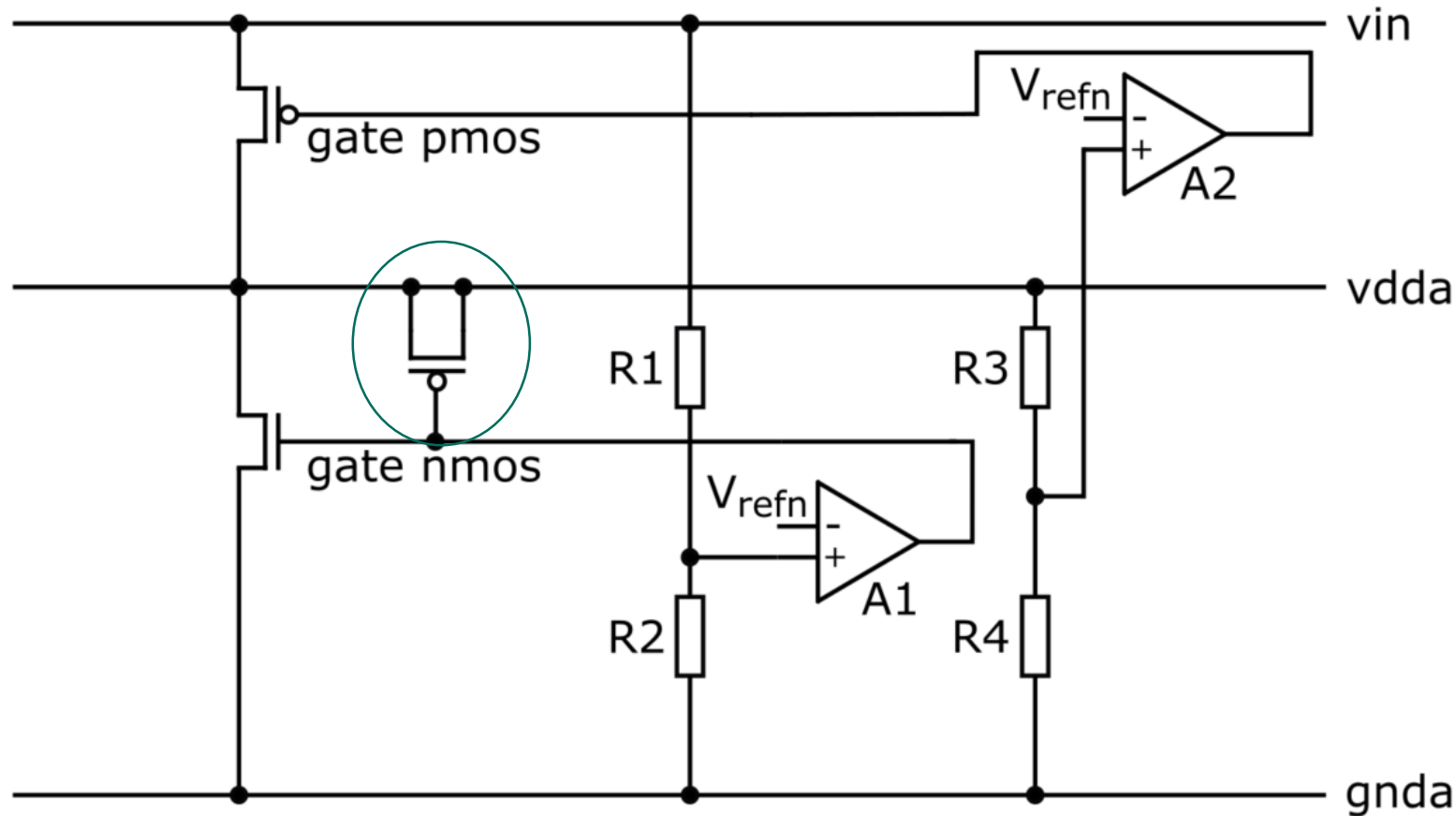


Stabilisation

Gate Kapazität = $7.75 \text{ fF}/\mu\text{m}^2$

hier 100 Transistoren mit $w = 10 \text{ }\mu\text{m}$
und $l = 10 \text{ }\mu\text{m}$

→ $C =$

Schematics of the power regulator

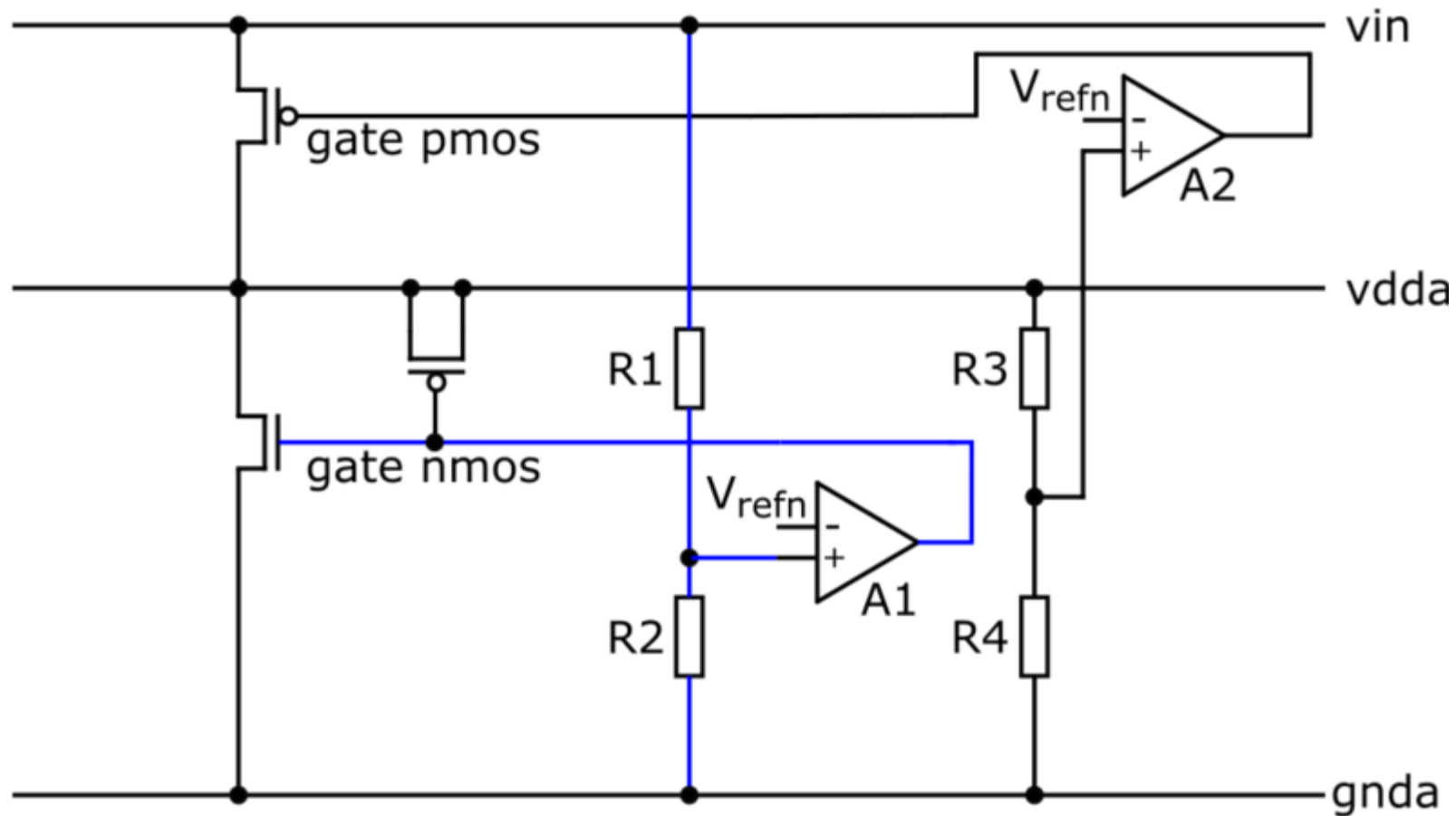


1. Regulation Loop

Out von A1 ändert sich mit vdda.

Bei Bedarf wird das „zu viel“ an Strom über Tn geleitet.

Ist vin zu hoch, leitet Tn mehr, ist vin „nah“ an vdda sperrt Tn.

Schematics of the power regulator

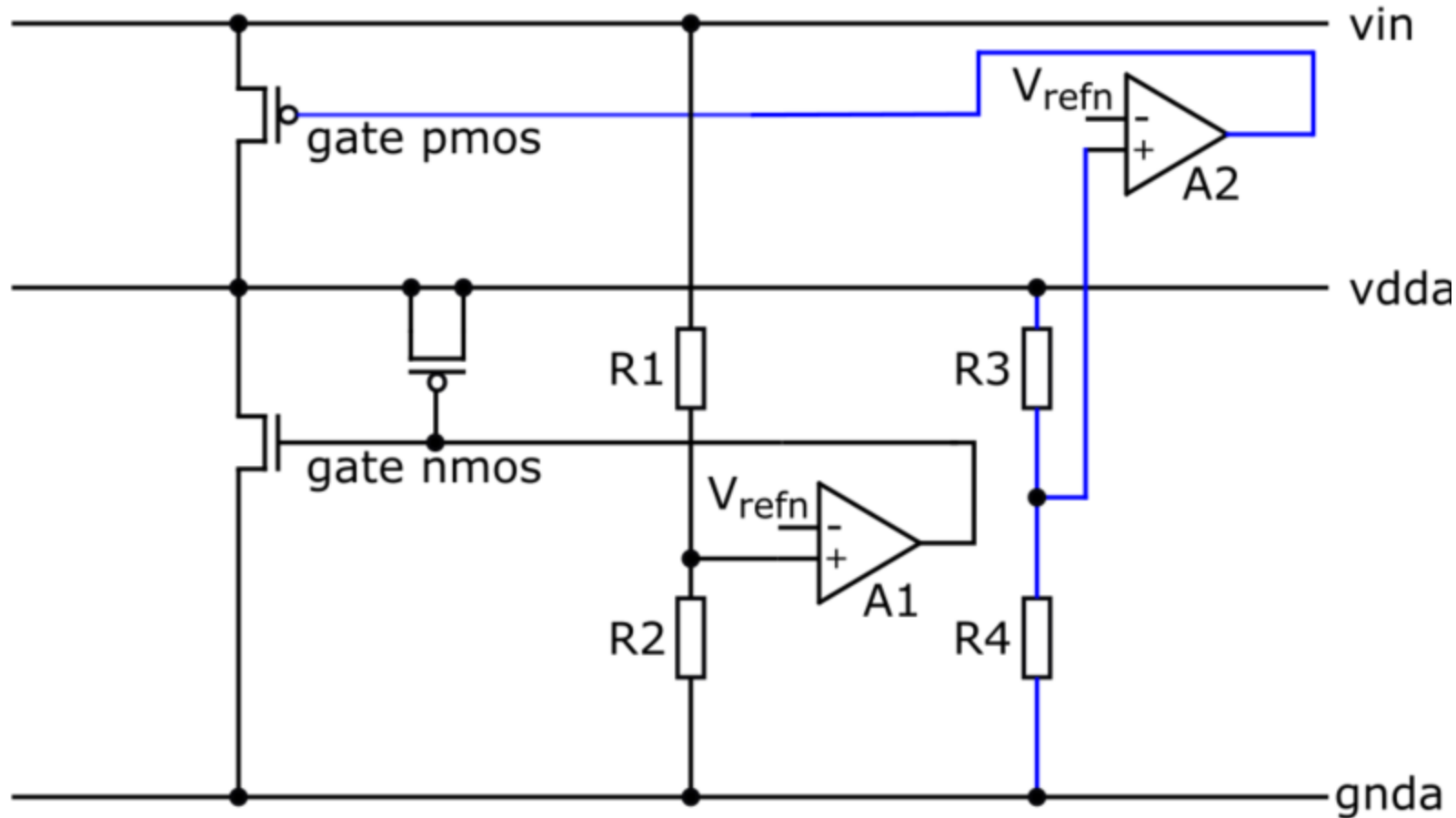


2. Regulation Loop

Out von A2 ändert sich mit vdda und steuert T_p an.

Wenn vdda zu hoch wird, schließt A2 T_p , vdda sinkt bis zum gewünschten Wert und T_p leitet wieder.

Test schematics similar to the one Michael Karagounis has shown

Parallel vs Serial Powering Scheme II


 


- Modules are connected in series
- Powered by constant current source
- Total supply current is defined by maximum load current of a single module
- Total supply voltage across the chain scales with the number of powered modules


$$\eta = \frac{1}{1 + \frac{R_C I_m}{n V_m}}$$

- Regulator circuitry required to generate constant supply voltage out of constant current

Test schematics for simulations

 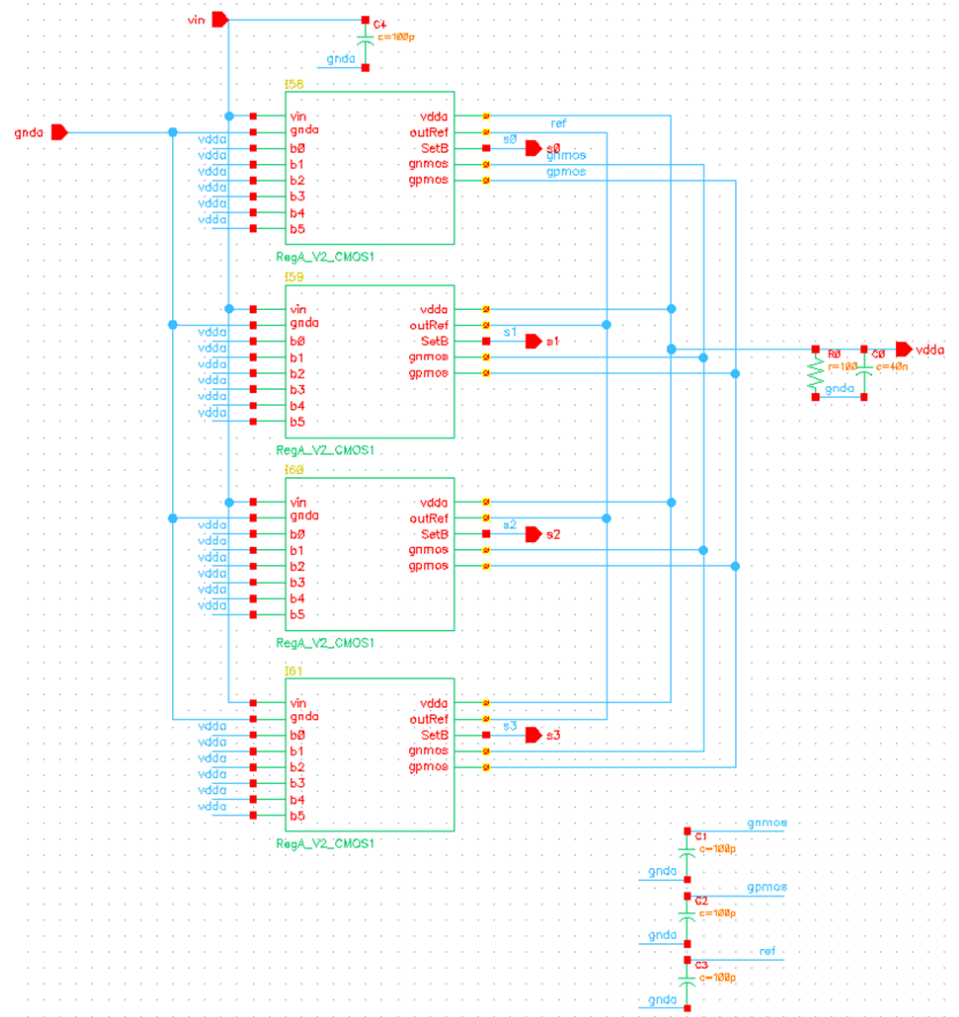


Test schematics for simulations

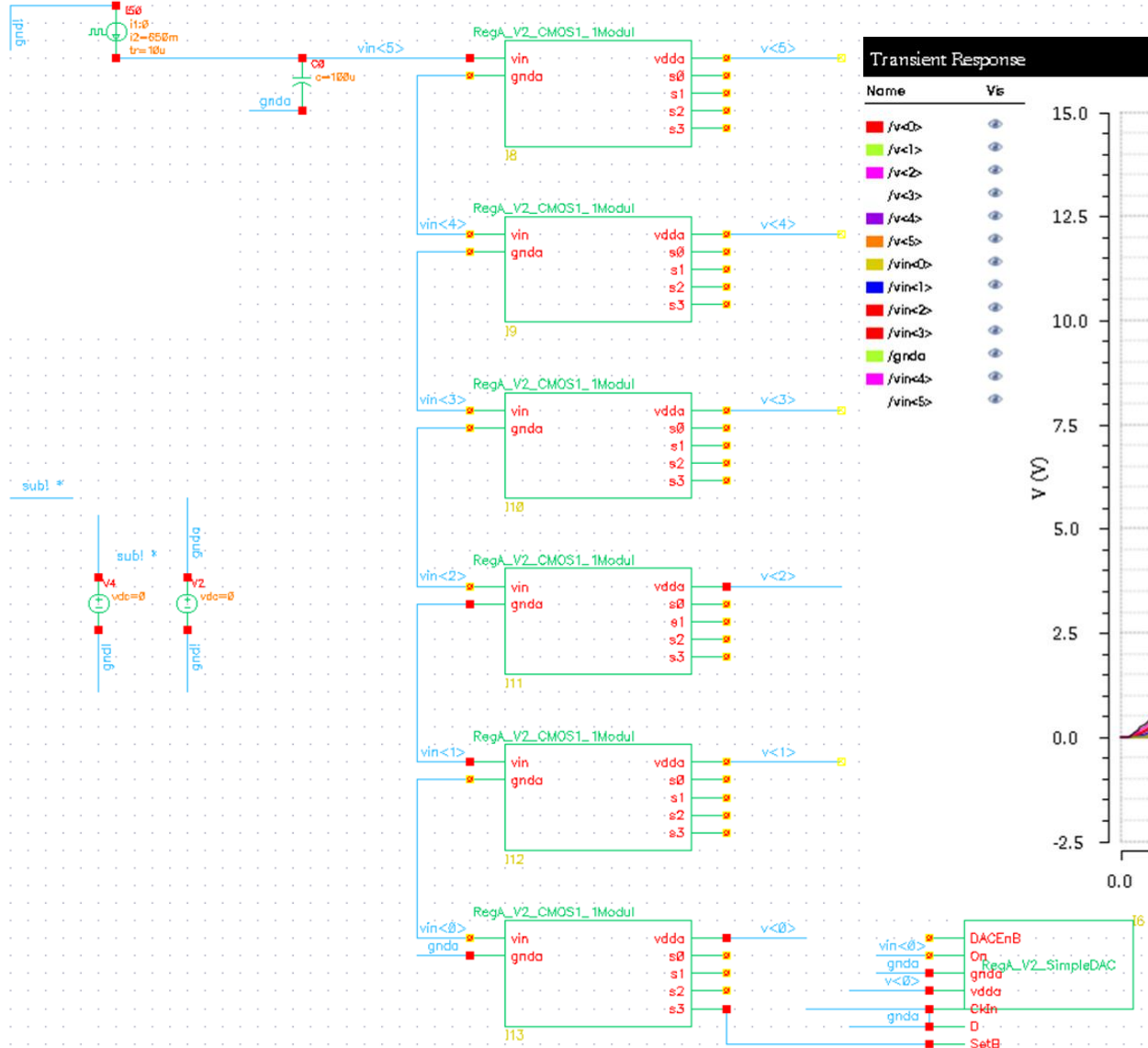

Transient Response


Name	Vis
/v<0>	●
/v<1>	●
/v<2>	●
/v<3>	●
/v<4>	●
/vin<0>	●
/vin<1>	●
/vin<2>	●
/vin<3>	●
/gnda	●
/vin<4>	●
/vin<5>	●

 

Layout Dimensions





- Layout of the control block

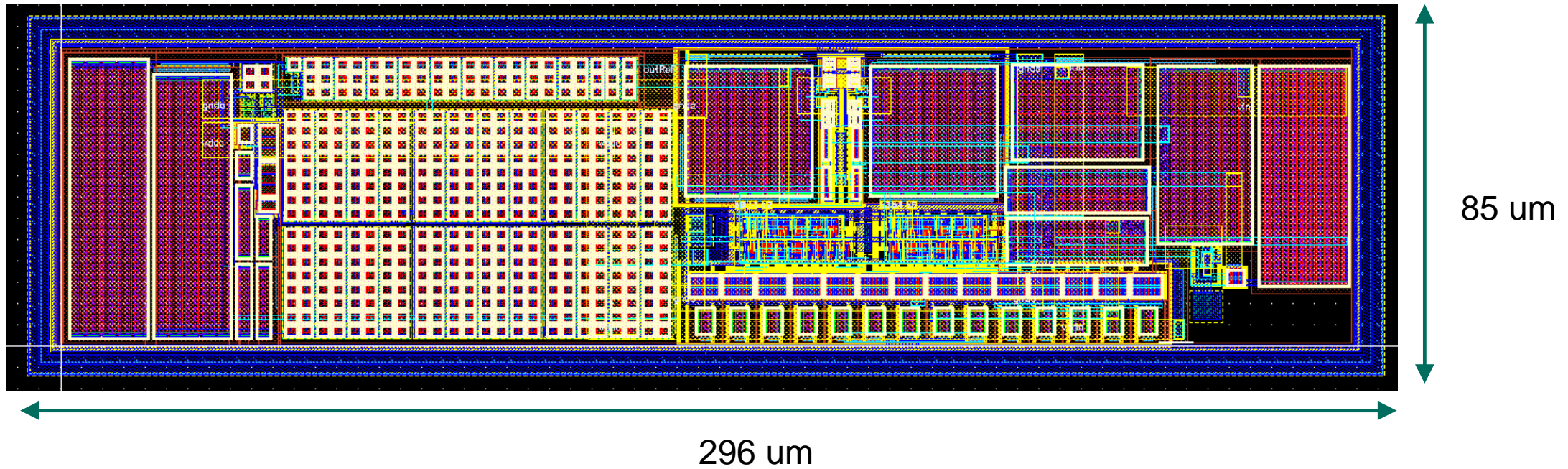

Layout Dimensions

  
- Tune Logic: 3 input bits to control 7 tune steps with identical resistors



Layout Dimensions



 - Big Transistors and stabilisation capacitor





UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386




Karlsruher Institut für Technologie

BACKUP

Serial Powering




■ Parallel Powering

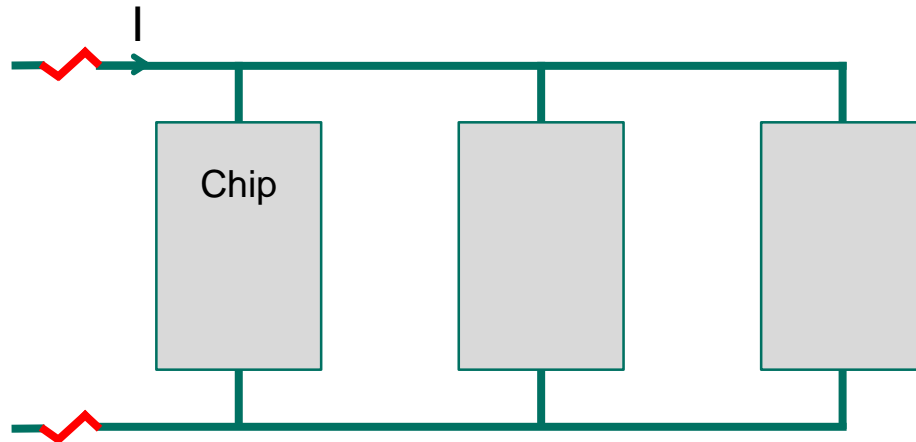

- chip connection parallel, all outputs on same voltage level

■ Serial Powering

 

- chip connection serial, all outputs on a different voltage level

Serial Powering




UNIVERSITÄT
HEIDELBERG
ZUKUNFT
SEIT 1386



Fachhochschule
Dortmund
University of Applied Sciences and Arts

Parallel vs Serial Powering Scheme I

 

- Modules are connected in parallel
- Powered by constant voltage source
- Total supply current scales with the number of modules
- Large supply currents affect efficiency
- IR drops on power cables

$$\eta = \frac{1}{1 + n \frac{I_m R_C}{V_m}}$$

- DC/DC conversion decreases supply current and increases efficiency
- DC/DC conv. has high material budget


22.02.2019

Shunt-LDO regulator in C65nm | RD53 General Meeting at RAL | michael.karagounis@hshl.de

Folie 23

Fachhochschule
Dortmund
University of Applied Sciences and Arts

Parallel vs Serial Powering Scheme II

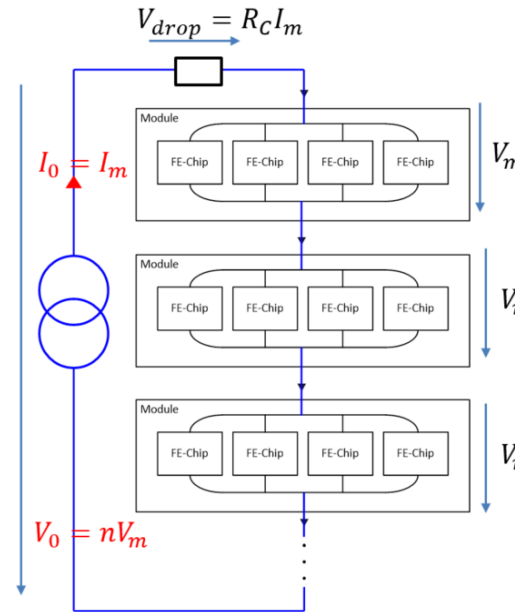

- Modules are connected in series
- Powered by constant current source
- Total supply current is defined by maximum load current of a single module
- Total supply voltage across the chain scales with the number of powered modules

$$\eta = \frac{1}{1 + \frac{R_C I_m}{n V_m}}$$

- Regulator circuitry required to generate constant supply voltage out of constant current

22.02.2019

Shunt-LDO regulator in C65nm | RD53 General Meeting at RAL | michael.karagounis@hshl.de

Folie 24

Overview of simulated circuits



Description of the circuit	Modification A	Modification B
FE-I 3 ATLAS hybrid pixel readout chip	Connection of transistor M1 changed	
LDO regulator with shunt (1)		
Regulator implemented on MuPix9		
Extended LDO regulator with shunt (2)	Modified circuit before A4, without A2	Like Modification A but with A2
Bandgap for reference voltage implemented on MuPix9		
Differential Amplifier implemented on MuPix9	Modified dimensions	

(1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009

(2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018

Overview of simulated circuits




Description of the circuit	Modification A	Modification B
FE-I 3 ATLAS hybrid pixel readout chip	Connection of transistor M1 changed	will be implemented on ATLASPix3
LDO regulator with shunt (1)		
Regulator implemented on MuPix9		
Extended LDO regulator with shunt (2)	Modified circuit before A4, without A2	Like Modification A but with A2
Bandgap for reference voltage implemented on MuPix9		
Differential Amplifier implemented on MuPix9	Modified dimensions	


(1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009

(2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018

FE-I 3 ATLAS hybrid pixel readout chip

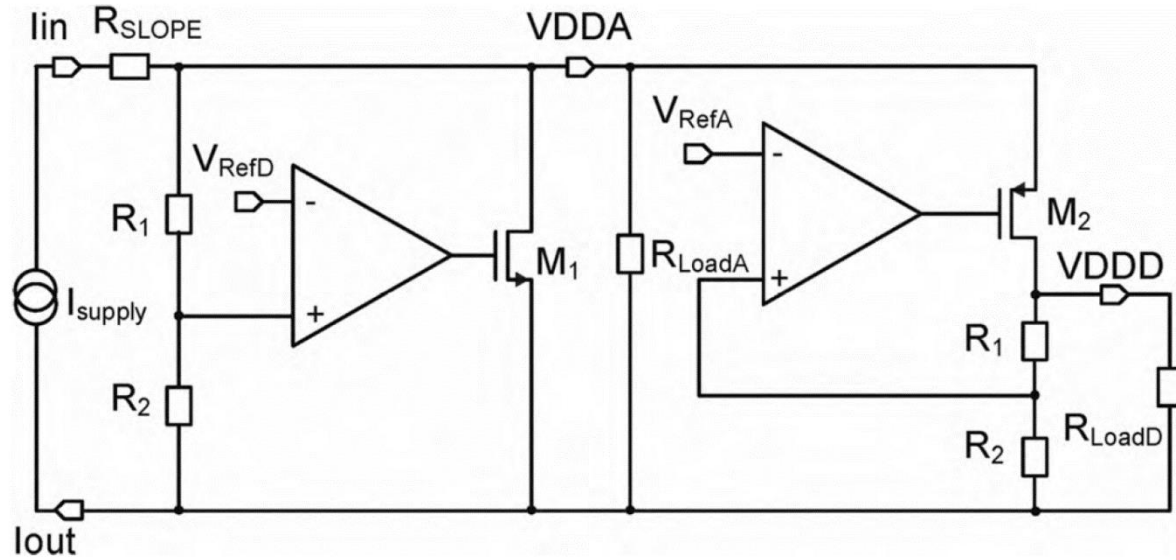

Power Regulator for ATLAS Pix3


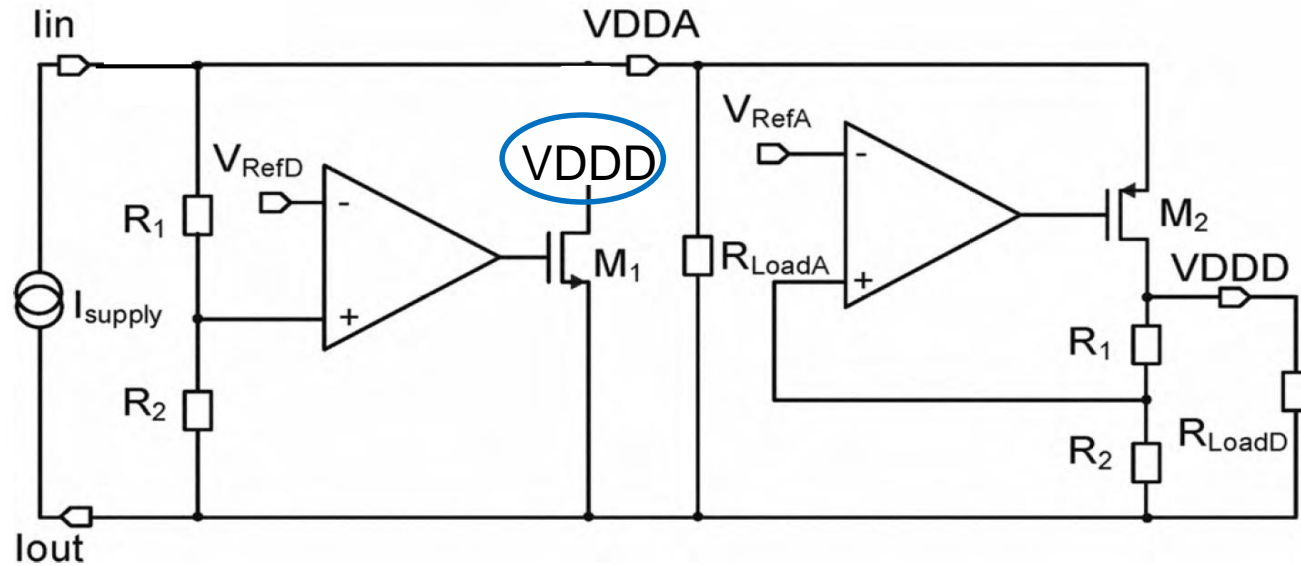


- $V_{DDA} = \sim 2.2 \text{ V}$
- $V_{DDD} = 1.8 \text{ V}$
- to protect M1 from too high voltages connected to VDDD

DC Analyse



 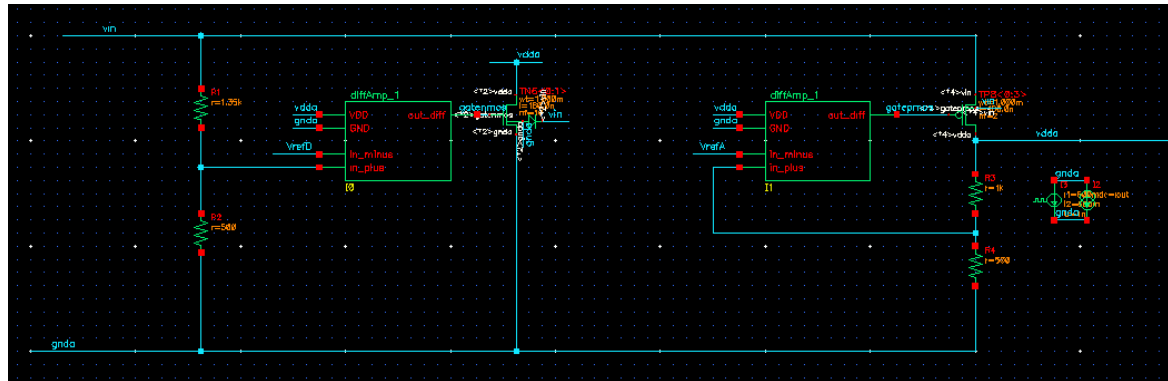
- $I_{in} = 520 \text{ mA}$ und I_{out} sweep $0 \dots 500 \text{ mA}$



DC Analyse





- lin sweep 20...500mA und Iout = 10mA

 

Transient Analyse




 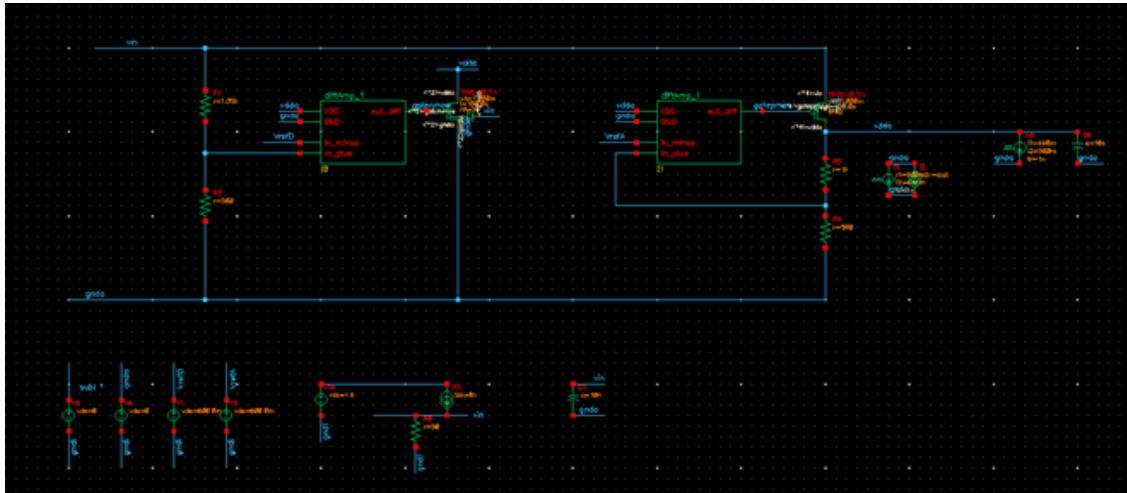- $I_{in} = 600 \text{ mA}$ and $I_{out} = I_{pulse} 490 \text{ mA} \rightarrow 500$



Power Regulator for ATLAS Pix3

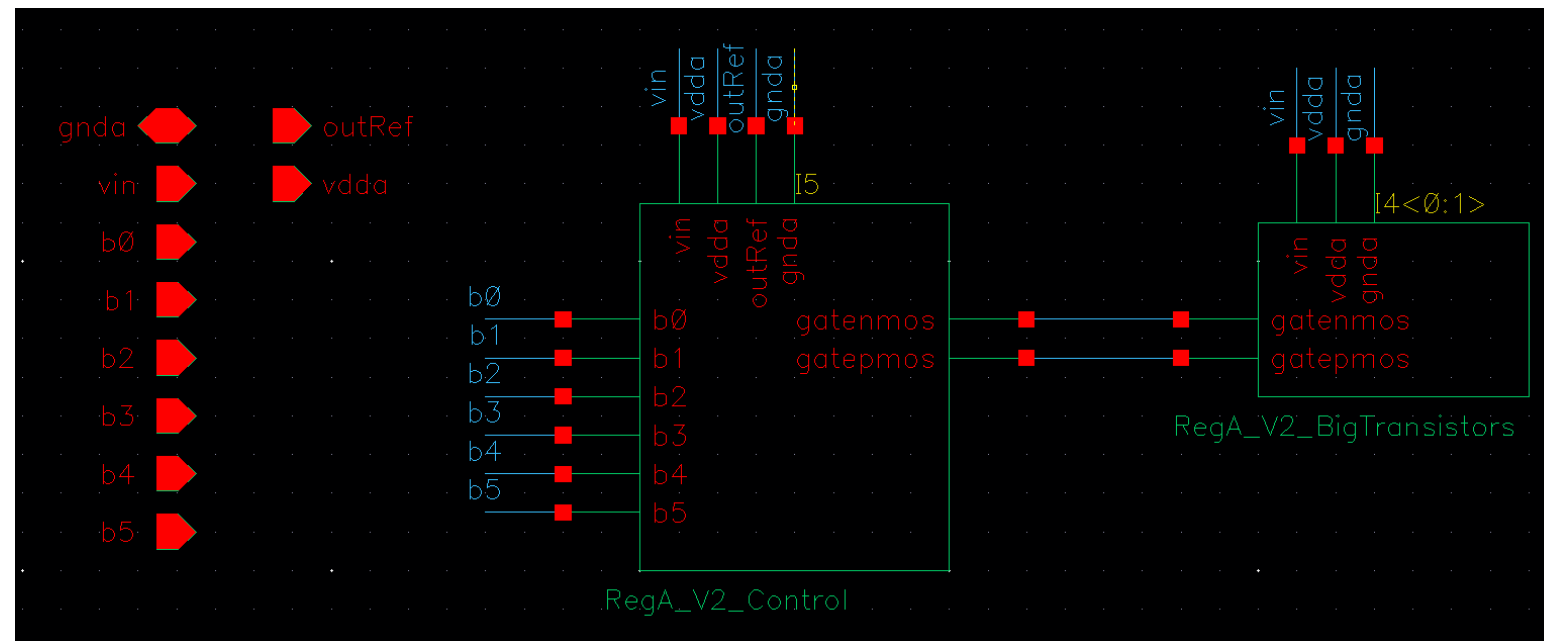
- Top schematic
- The circuit is split in 3 parts:
 - Control block
 - two times the same block with the big power transistors



Power Regulator for ATLAS Pix3




■ Schematic of the control block

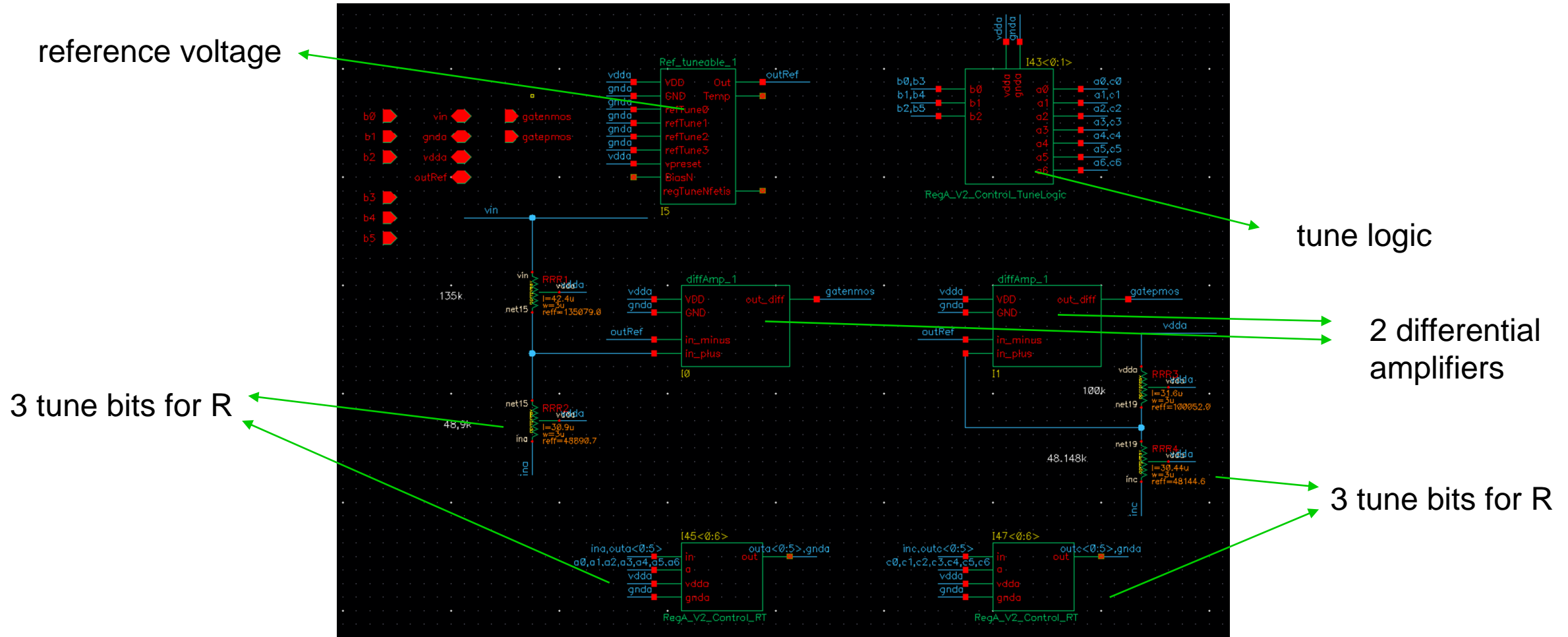

Power Regulator for ATLAS Pix3





- Layout of the control block


 


Power Regulator for ATLAS Pix3

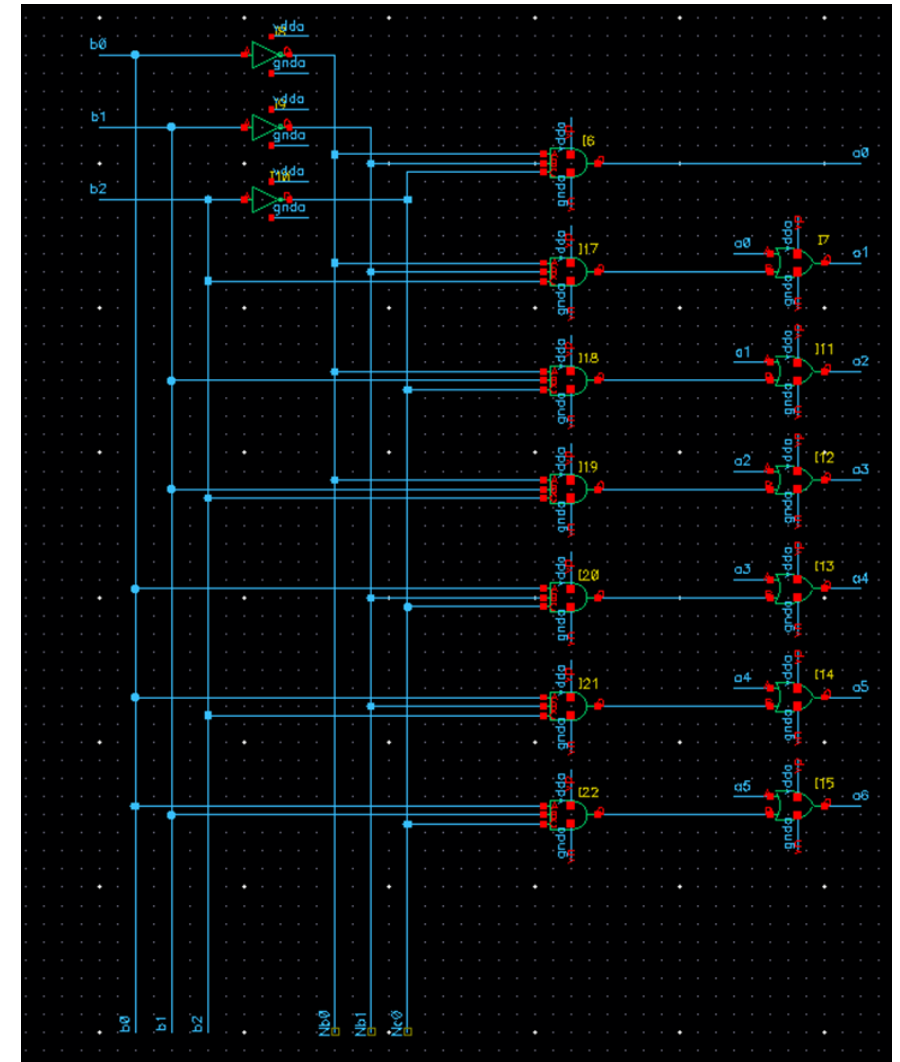
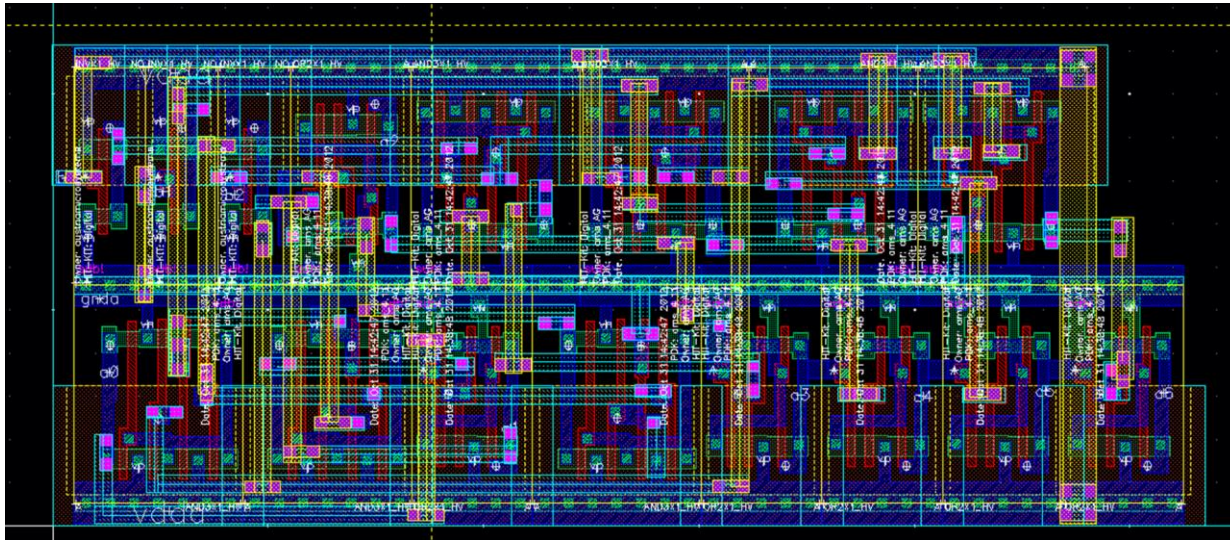
- Tune Logic: 3 input bits to control 7 tune steps with identical resistors



Regulator implemented on MuPix9

 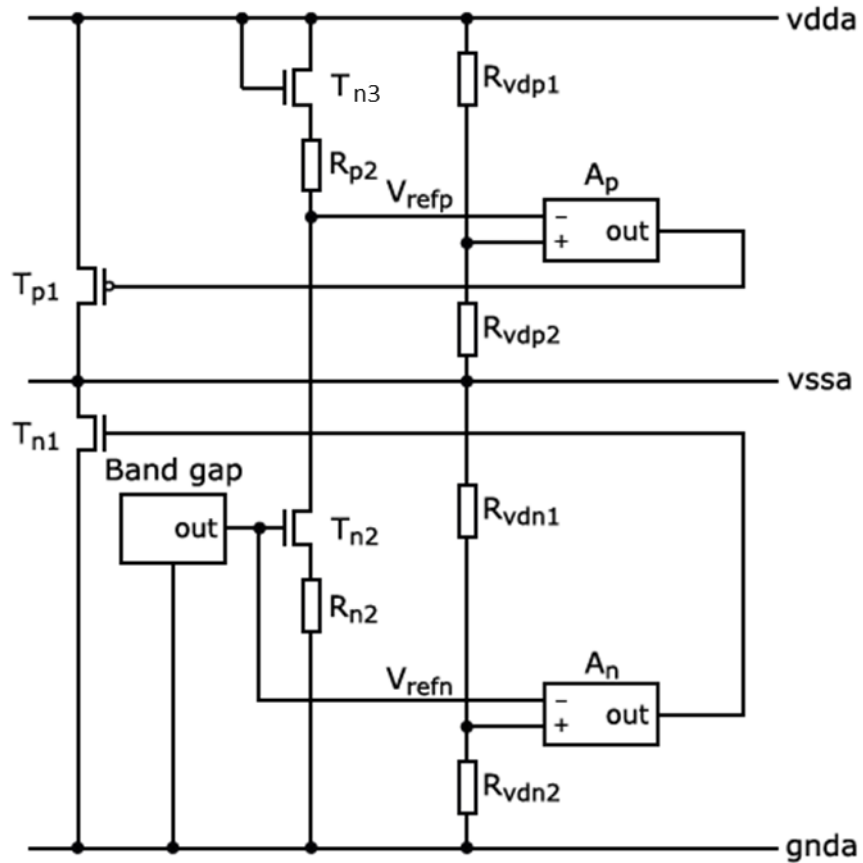


LDO regulator with shunt (1)

 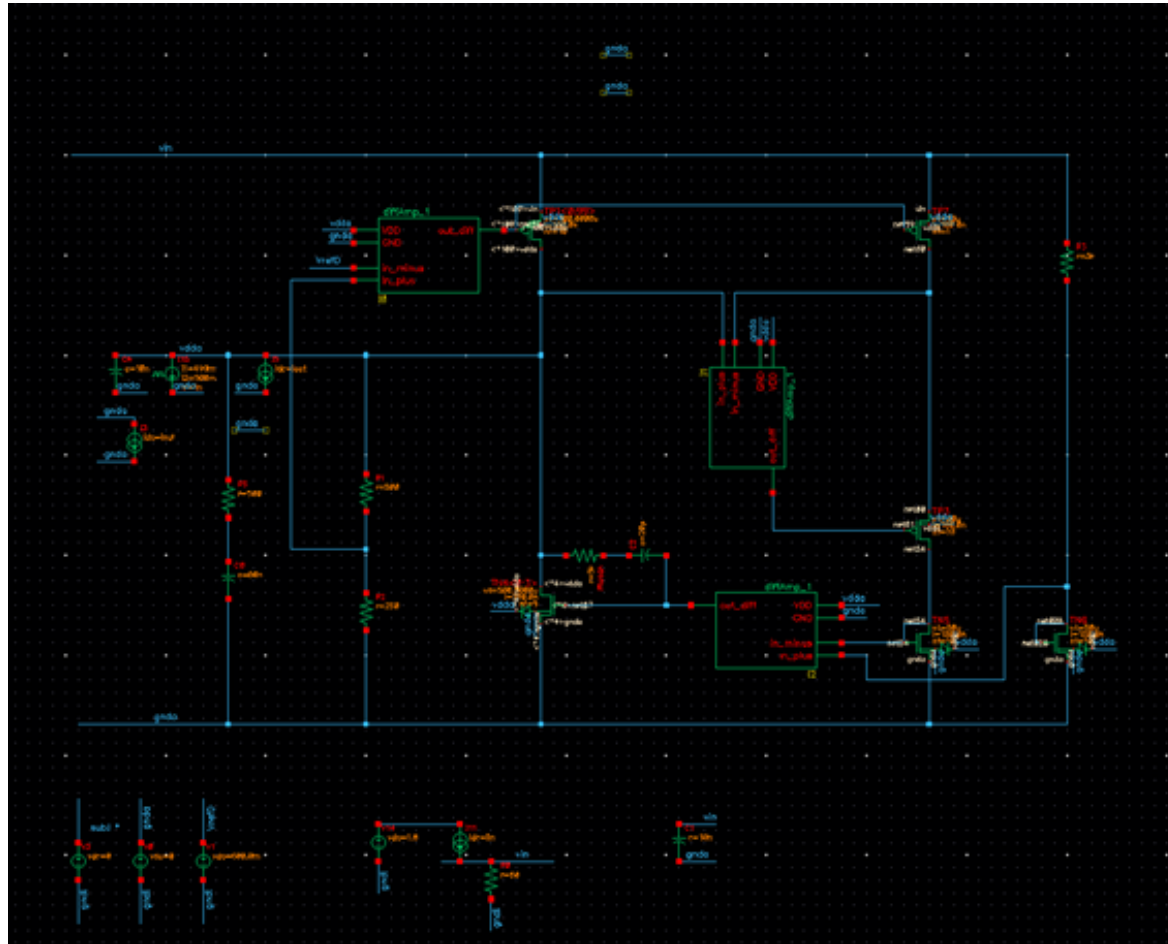

- (1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009
- (2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018

Modified LDO regulator with shunt (2)

- Modified circuit before A4, without A2


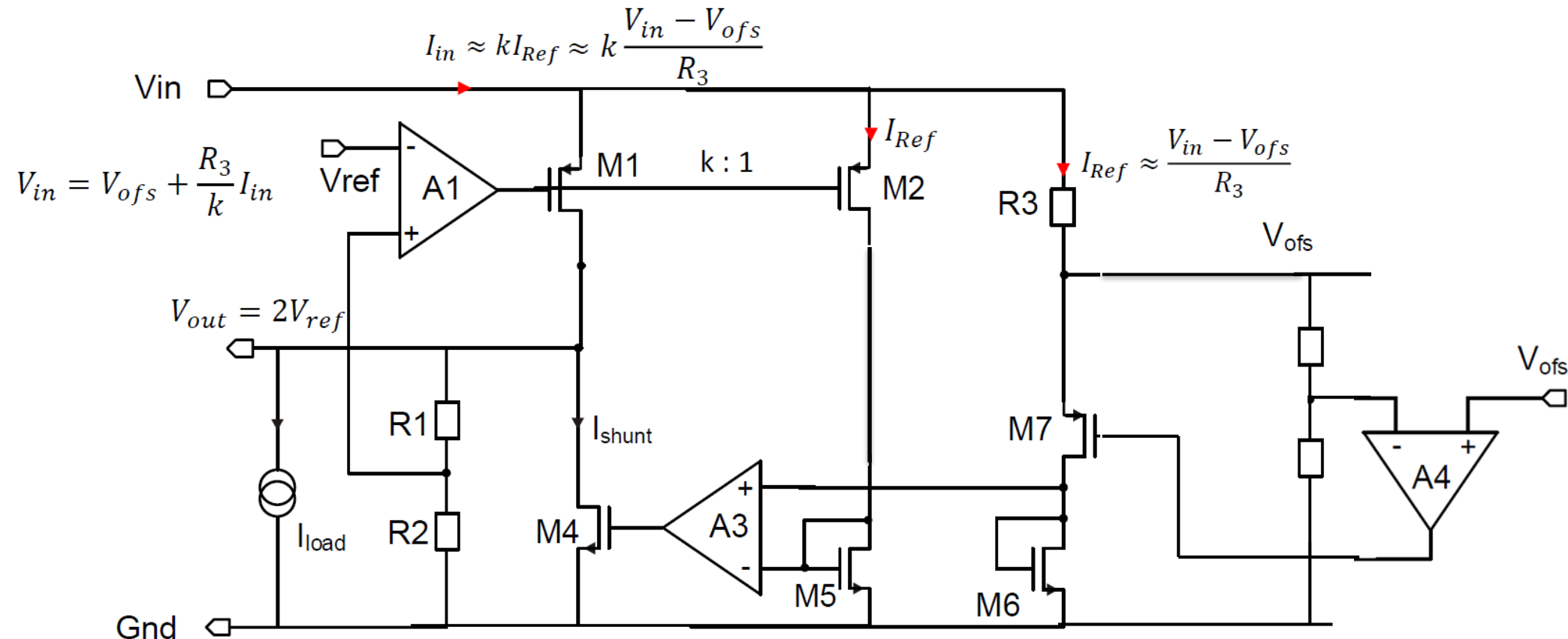


- (1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009
- (2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018

Modified LDO regulator with shunt (2)





- Modified circuit before A4, without A2

 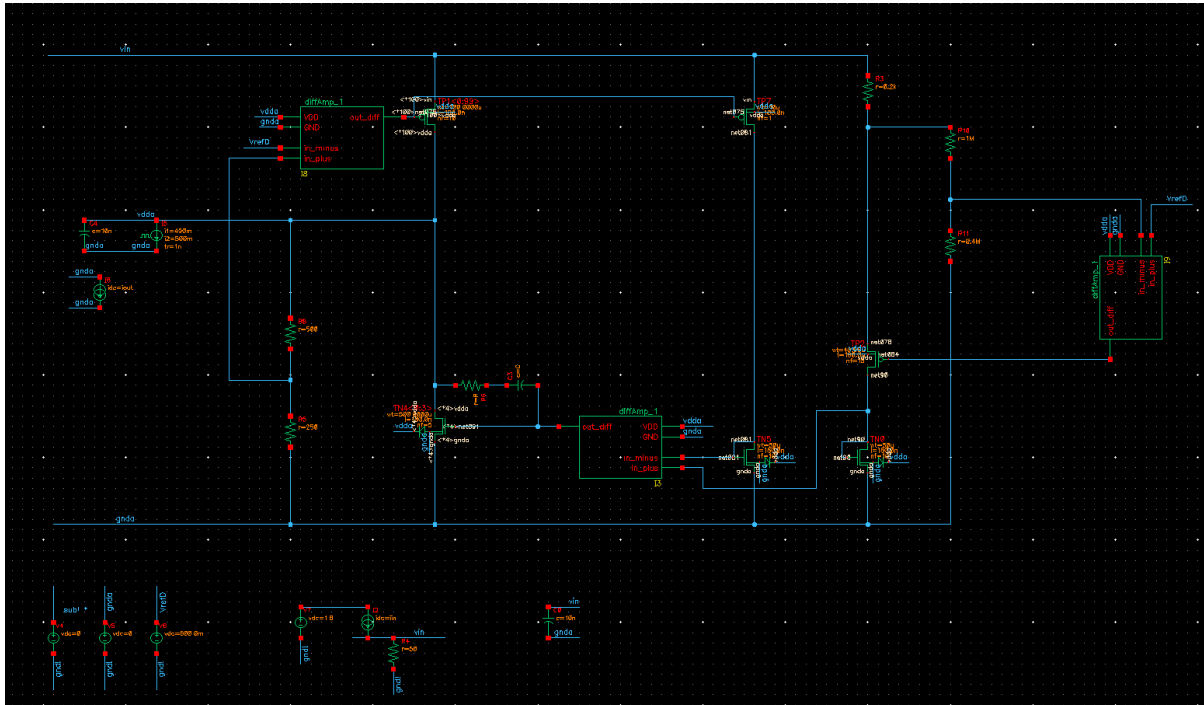

- (1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009
- (2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018

Modified LDO regulator with shunt (2)


- Modified circuit before A4, without A2

 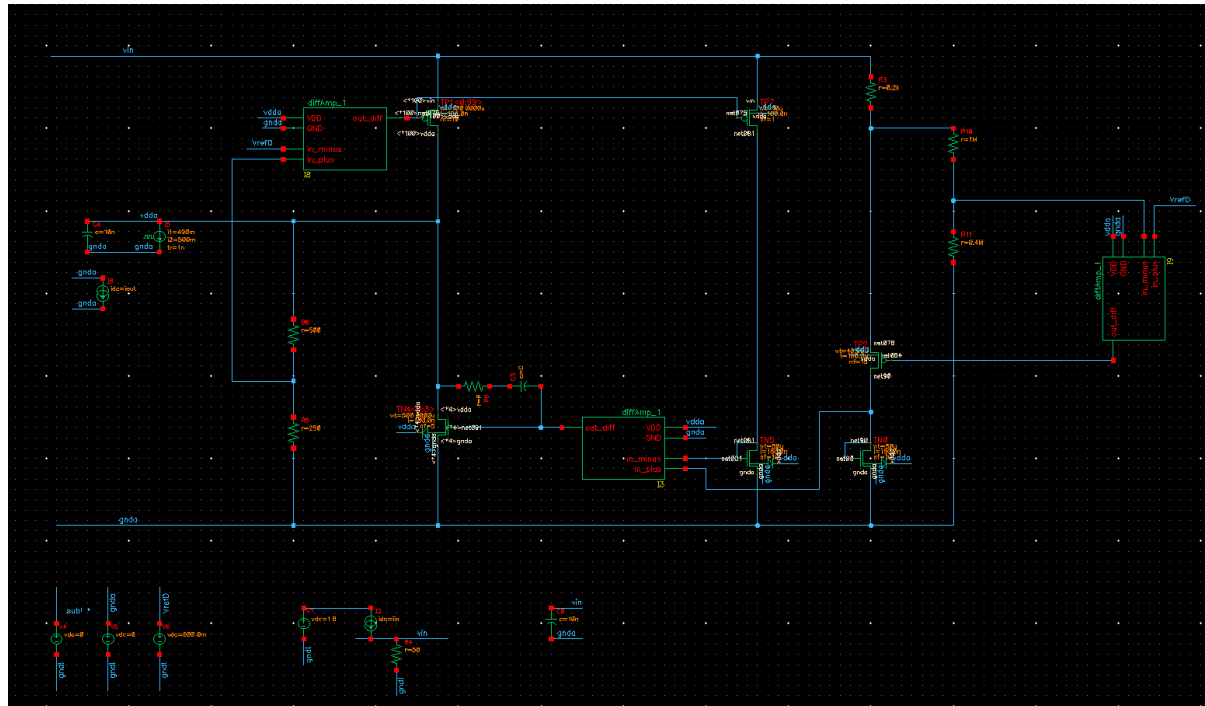

- (1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009
- (2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018


Modified LDO regulator with shunt (2)

- Modified circuit before A4, with A2

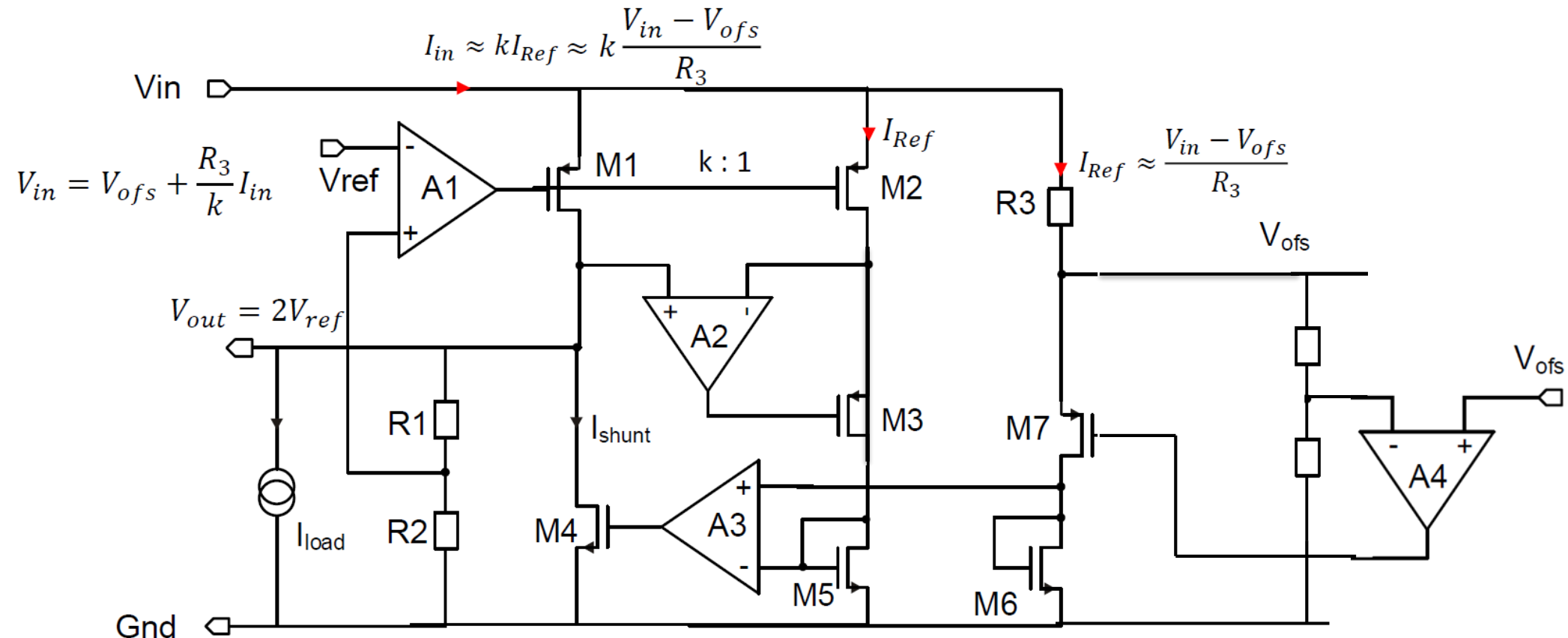

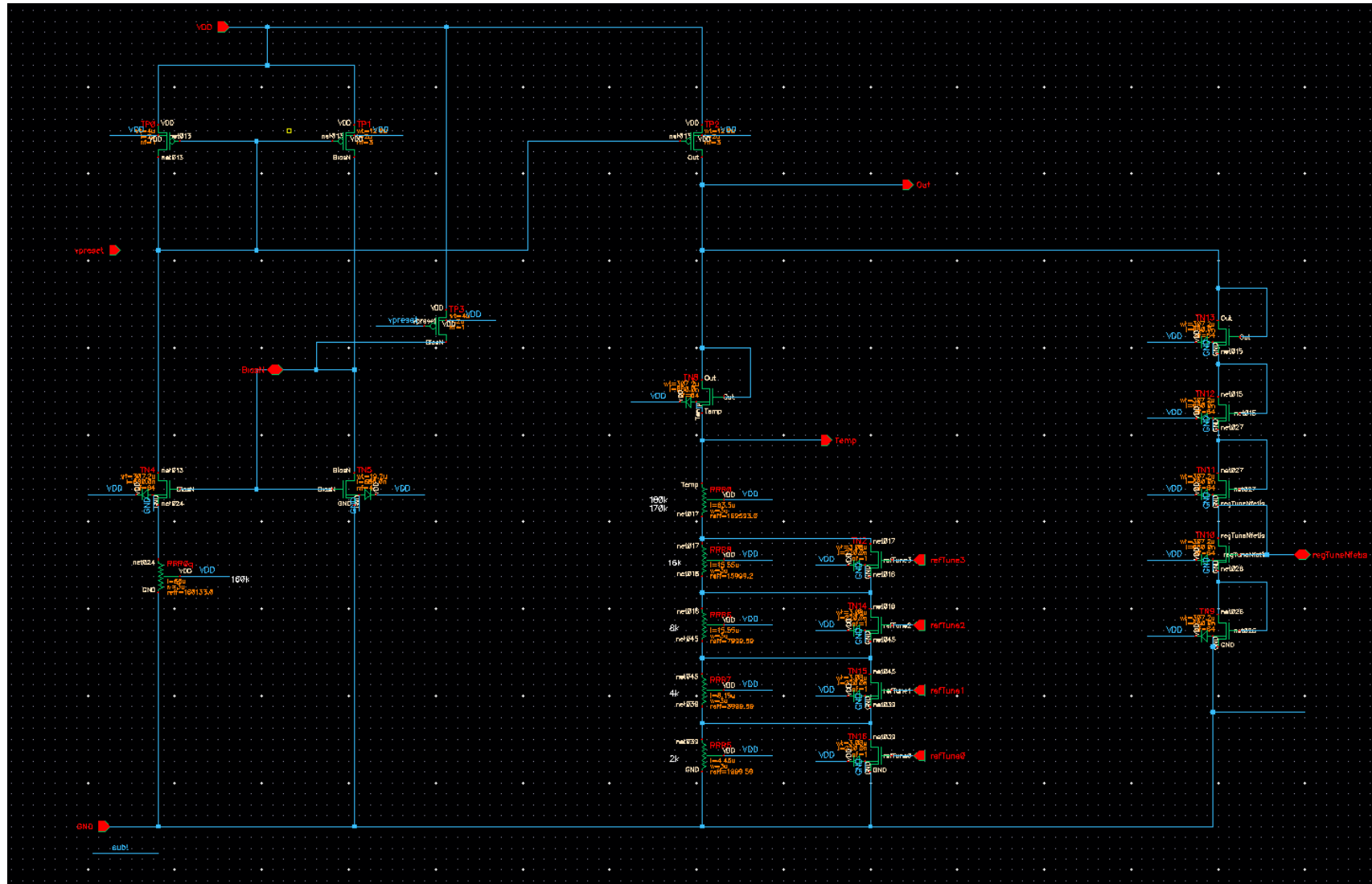- (1) Michael Karagounis et al., "An Integrated Shunt-LDO Regulator for Serial Powered Systems", Proceedings of ESSCIRC, 2009
- (2) Michael Karagounis, "Serial Powering with the Shunt-LDO Regulator", ATLAS Upgrade Week, 16.04.2018

Bandgap for reference voltage implemented on ATLAS Pix3



Measurements with Power Regulator on MuPix9

 


Fig. 1: The regulator's output voltage is flat in a wide range of VDD


 


Fig. 2: Tune bits can fine tune the regulator's output voltage

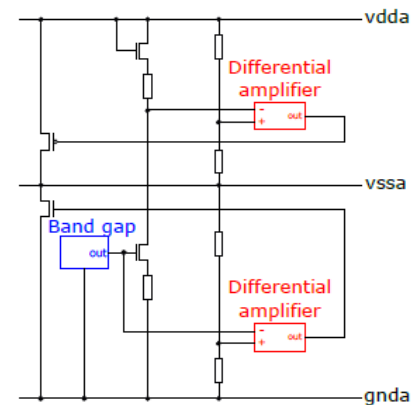

Schematic of the power regulator used in MuPix9

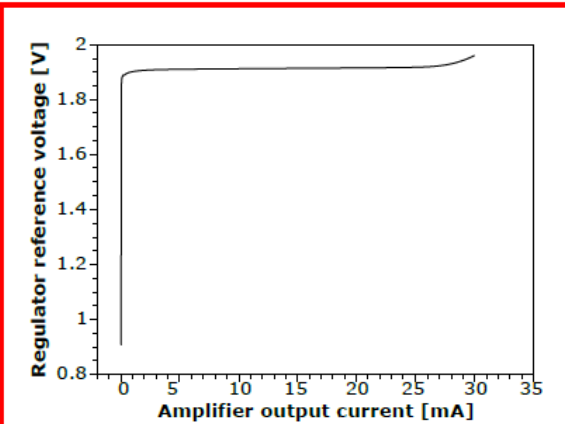


Fig. 3: The amplifier provides a stable voltage for a wide current range



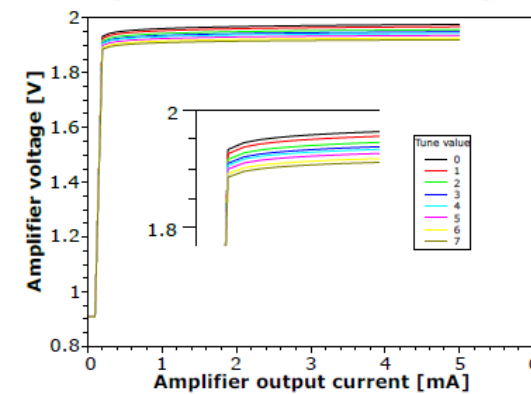


Fig. 4: Tune bits can fine tune the amplifier's output voltage

Power Regulator for ATLAS Pix3

 


■ RT Block

 

Power Regulator for ATLAS Pix3


- Big Transistors

 

Modified LDO regulator with shunt (2)




- Modified circuit before A4, with A2

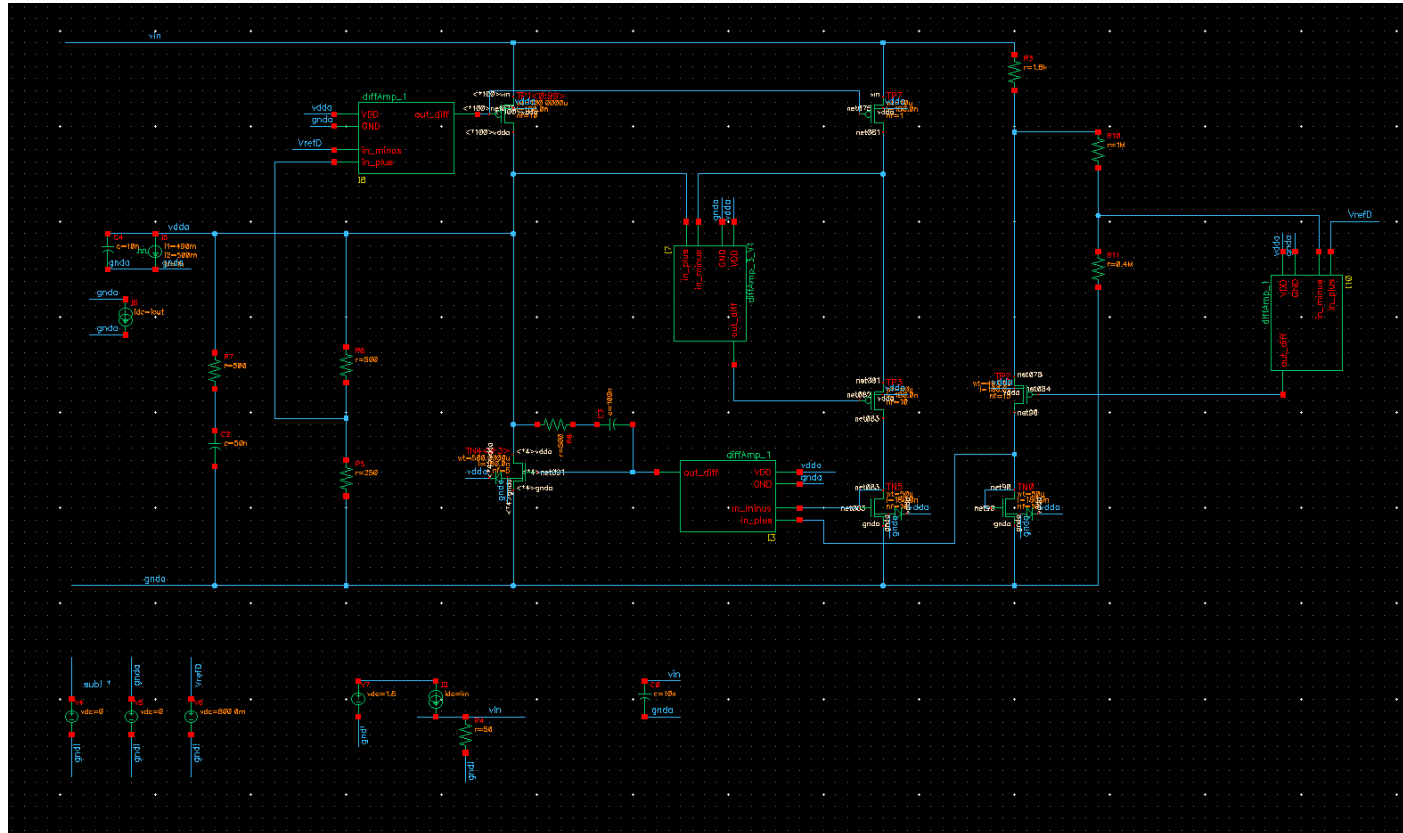

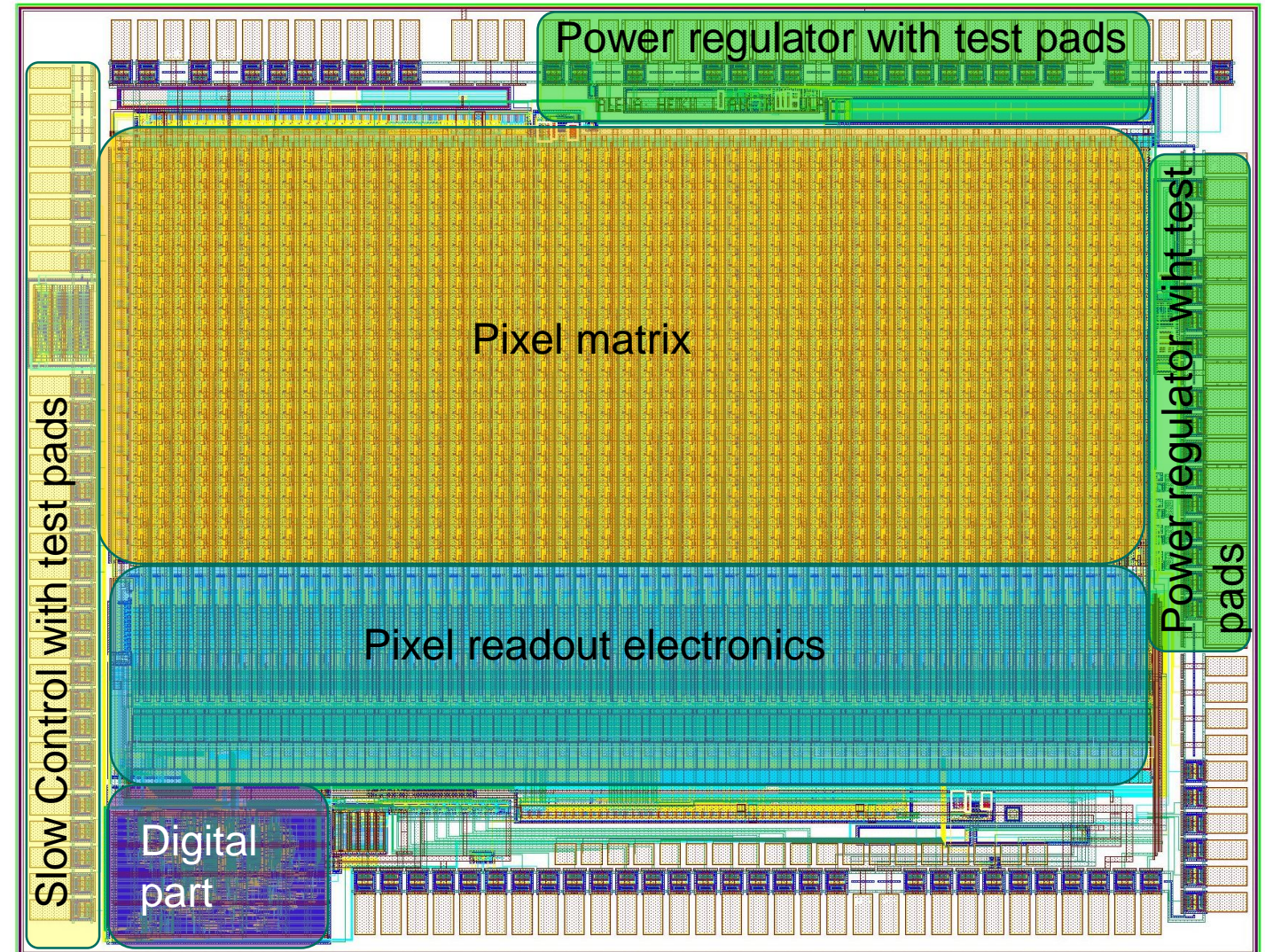- (1) Michael Karagounis et al., “An Integrated Shunt-LDO Regulator for Serial Powered Systems”, Proceedings of ESSCIRC, 2009
- (2) Michael Karagounis, “Serial Powering with the Shunt-LDO Regulator”, ATLAS Upgrade Week, 16.04.2018



Overview of the MuPix9

- Small sensor prototype (4700 μm x 3600 μm)
- AMS aH18 HV-CMOS
 - Minimal gate length of 180nm
 - Substrate with 20 Ωcm
 - 48 columns each with 20 pixels
- Main parts:
 - Pixel matrix
 - Pixel readout electronics
 - Digital part with slow control
 - Slow control as stand-alone part
 - Two power regulators



Overview of the MuPix9

  
- Changes in comparison to MuPix8
 - one pixel matrix
 - Pixels in NMOS instead of PMOS
 - Readout cells are modified: now with capacitor for capacitive coupling for serial powering. Three modes concept from MuPix8 is kept.



- Digital part with modified state machine and new slow control
- slow control as stand-alone part

Regulator Element

 
- Same element with very small modifications for every solution
- Very small temperature dependency
- 8 tune bits
- Actual design as simple as possible, without linear regulator and as less space consuming as possible



Regulator Element



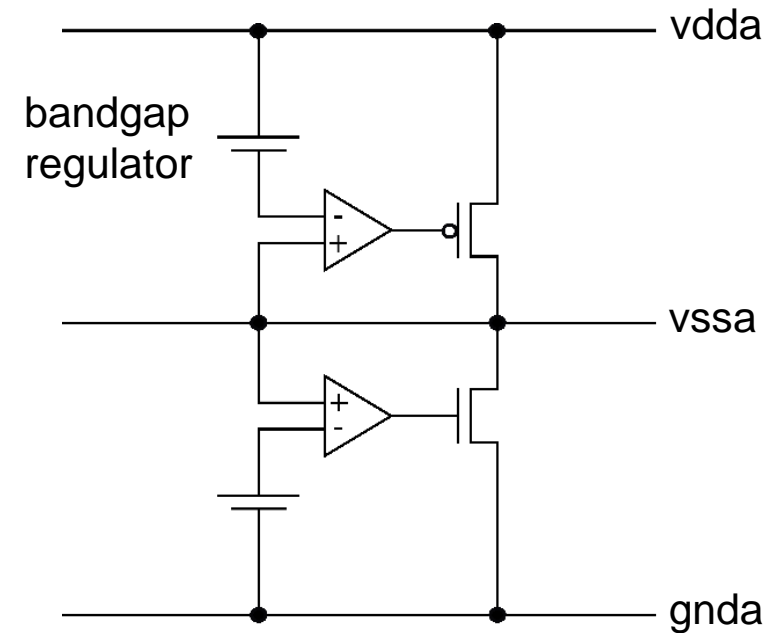
- Same element with very small modifications for every solution
- Very small temperature dependency
- 8 tune bits
- Actual design as simple as possible, without linear regulator and very compact
- Functional concept is shown here:
 - bandgap regulator works like a battery, which supply a fixed current
 - in real circuit only one bandgap, current is mirrored
 - two differential amplifiers



Serial powering – Introduction to standard concepts




■ Parallel Powering

 

- chip connection parallel, all outputs on same voltage level

■ Serial Powering

 


- chip connection serial, all outputs on a different voltage level

Serial powering – Introduction to HVCMOS concepts




■ Parallel Powering

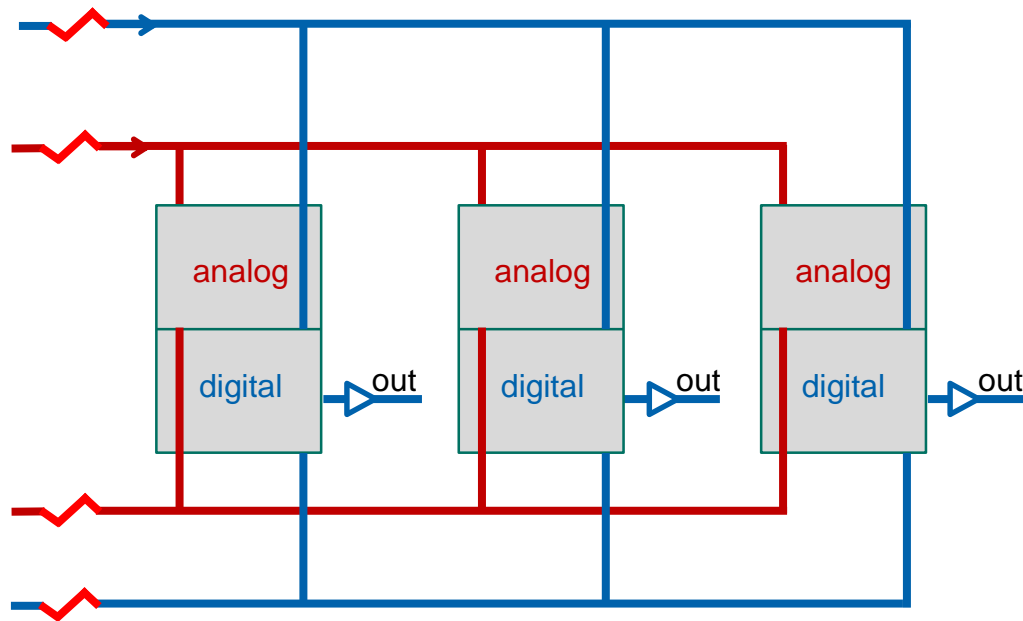

- Analog and digital powering separated in two circuits
- All digital levels are the same

■ Serial Powering

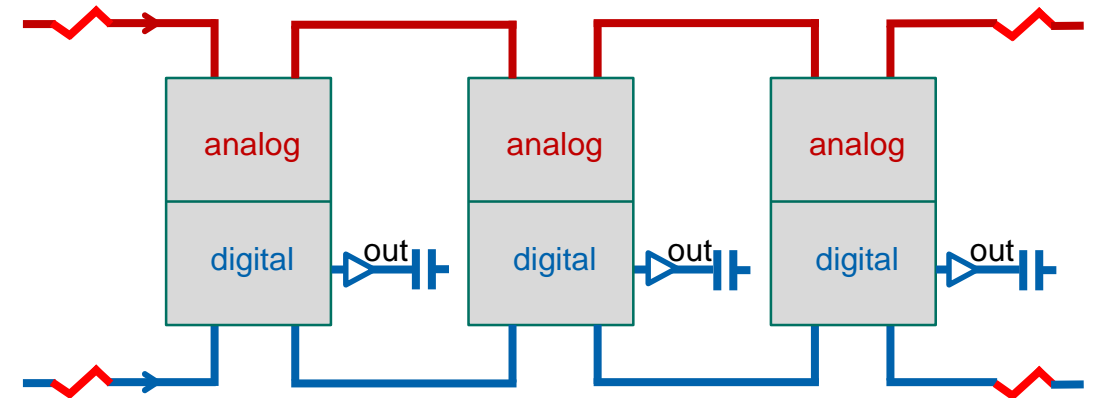


- chip connection serial, all outputs on a different voltage level
- Solution: conductive coupling

Chip interconnection concepts for serial powering

Concept 1: vdda and vssa separated



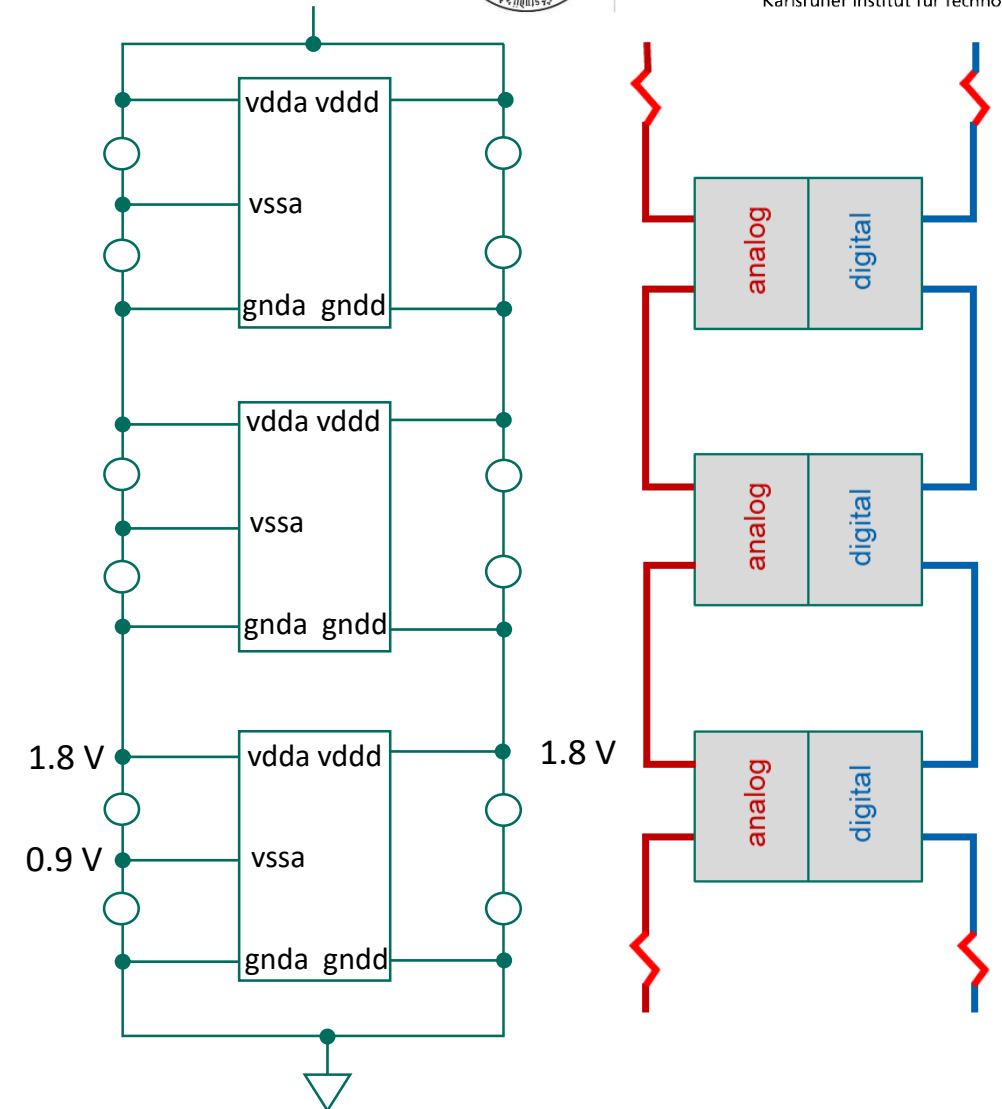- Analog and digital voltage separated for lower noise
- Analog part with vdda (1.8 V) and vssa (0.9 V)
- Regulator element represented with two circles




Chip interconnection concepts for serial powering

Concept 2: $v_{dda} = v_{ssa}$



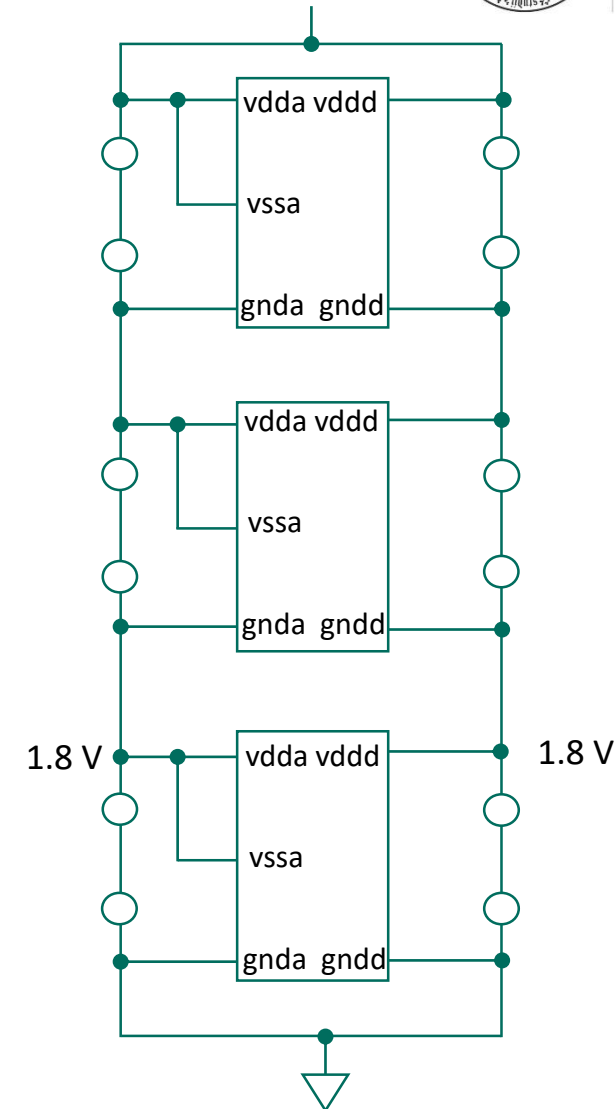
- Similar to concept 2, but:
- $v_{ssa} = v_{dda} = 1.8\text{ V}$
- Redesign of pixel amplifier necessary



Chip interconnection concepts for serial powering

Concept 3: shared voltage

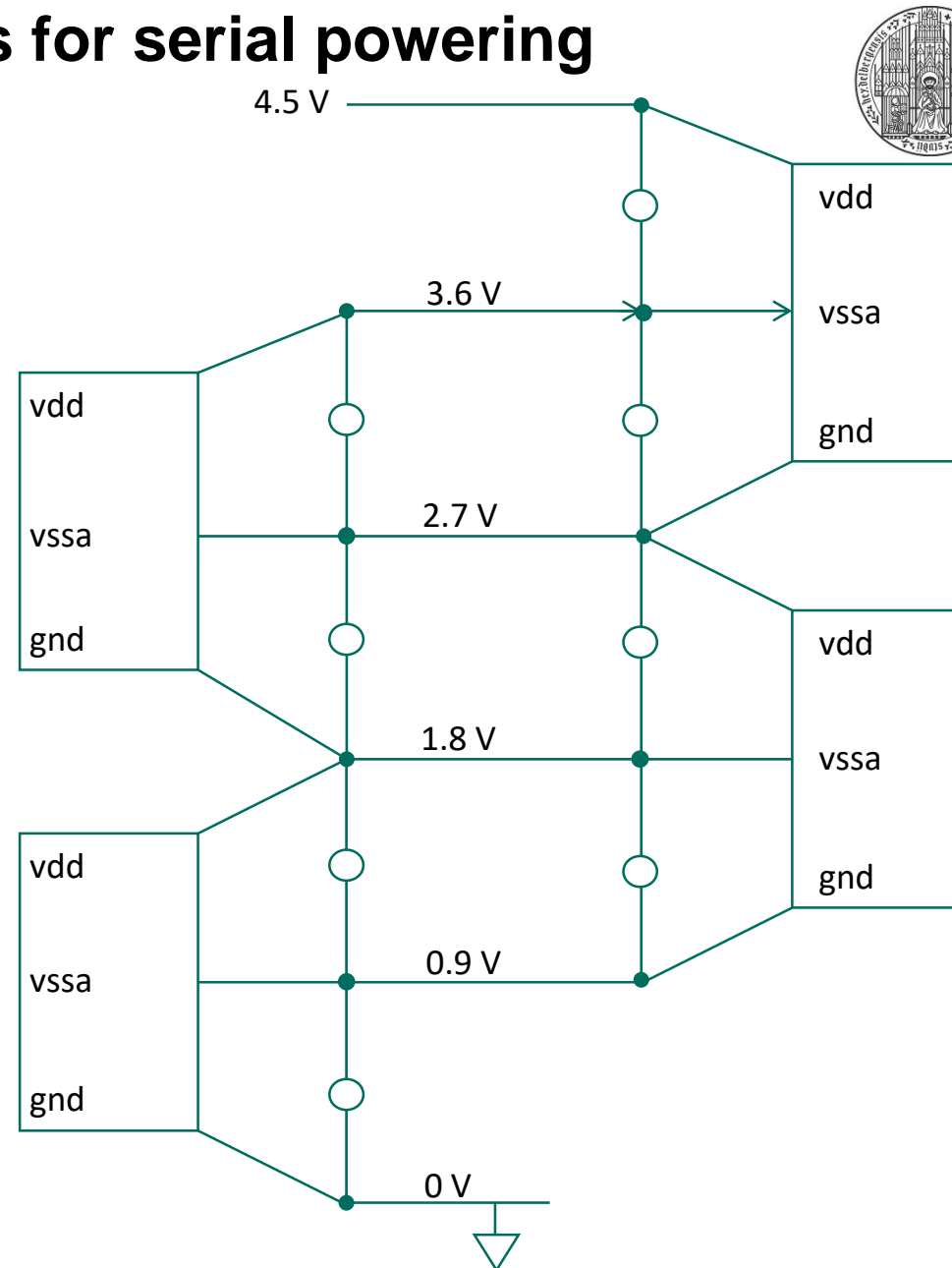- Lower input current
- Less power consumption
- “Shared voltage”




Chip interconnection concepts for serial powering

Concept 4: analog part serial, digital part parallel



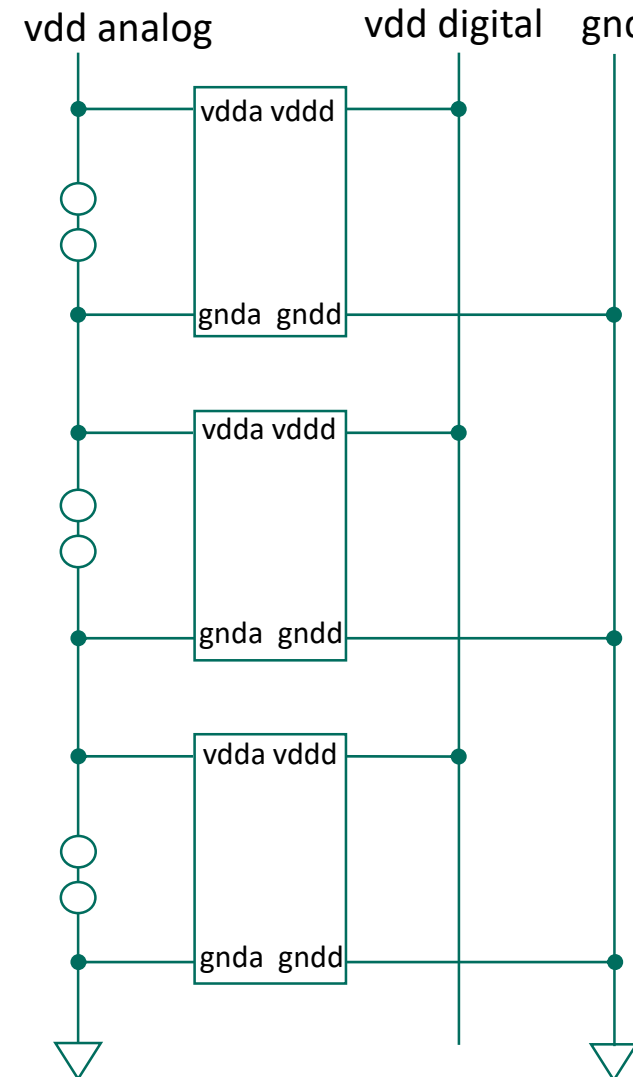- Analog and digital voltage separated
- Analog part serial, digital part parallel
- For analog part all concepts that were presented can be used




Vision for next generation MuPix



- On a full-size MuPix: three submatrices similar to MuPix8, but every submatrix identical
 - submatrices powered in serial
 - digital and analog power disconnected and captive coupled
 - chips powered in parallel
 - leads to a current reduction of 2/3

3 submatrices
parallel powered

 

3 submatrices
serial powered

